



SWINBURNE
UNIVERSITY OF
TECHNOLOGY


COS10004 Computer Systems

Lecture 3: Counters and Shift Registers

CRICOS provider 00111D

Dr Chris McCarthy

Building a computer? Things we need:

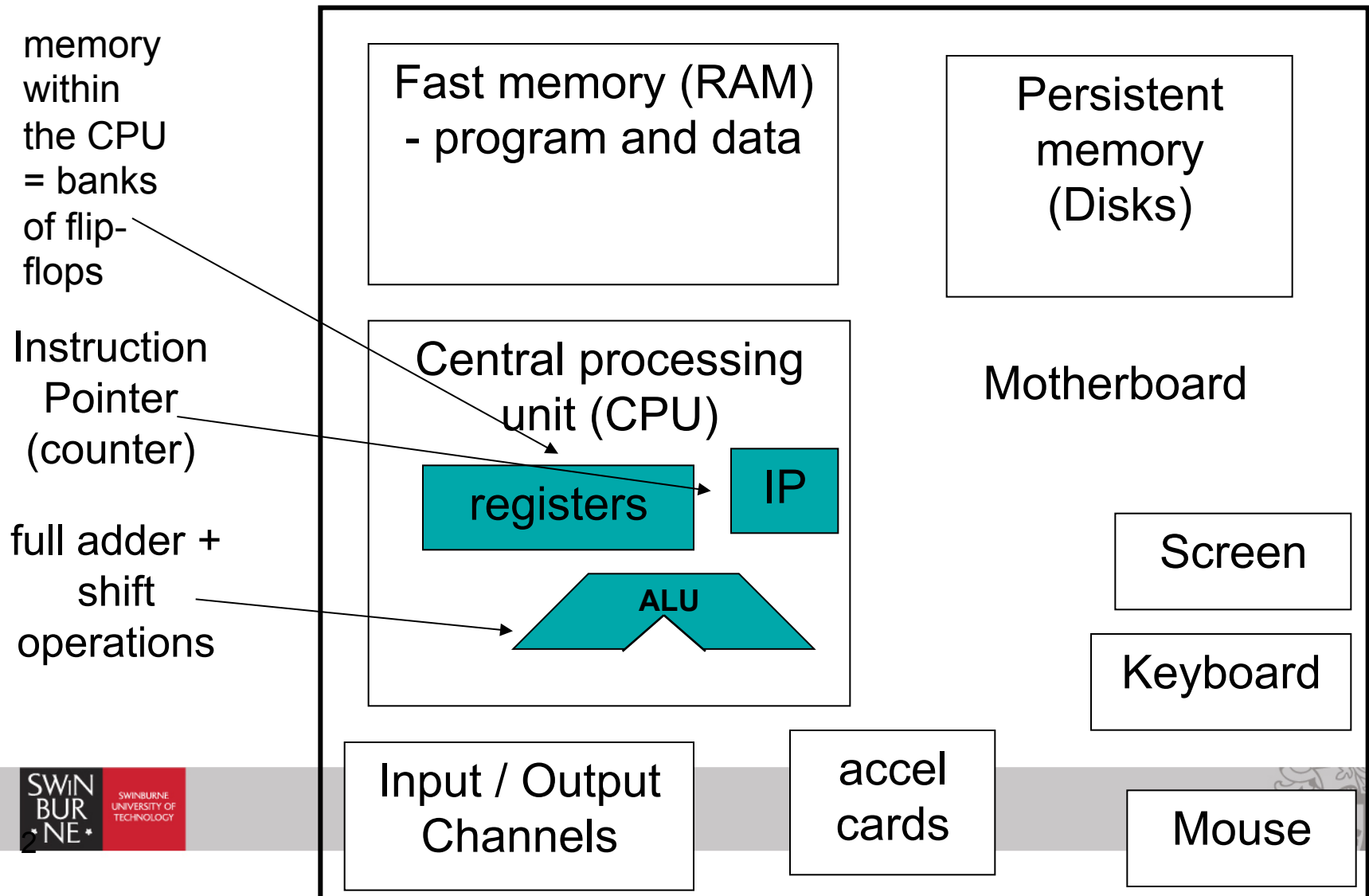


REGISTERS

Fast RAM (uses transistor states)

- > Uses clocked flip-flops
- > Inside the CPU chip
- > Limited number of them (cause it's hardware)
- > Let's build one...


D-TYPE FLIP-FLOP

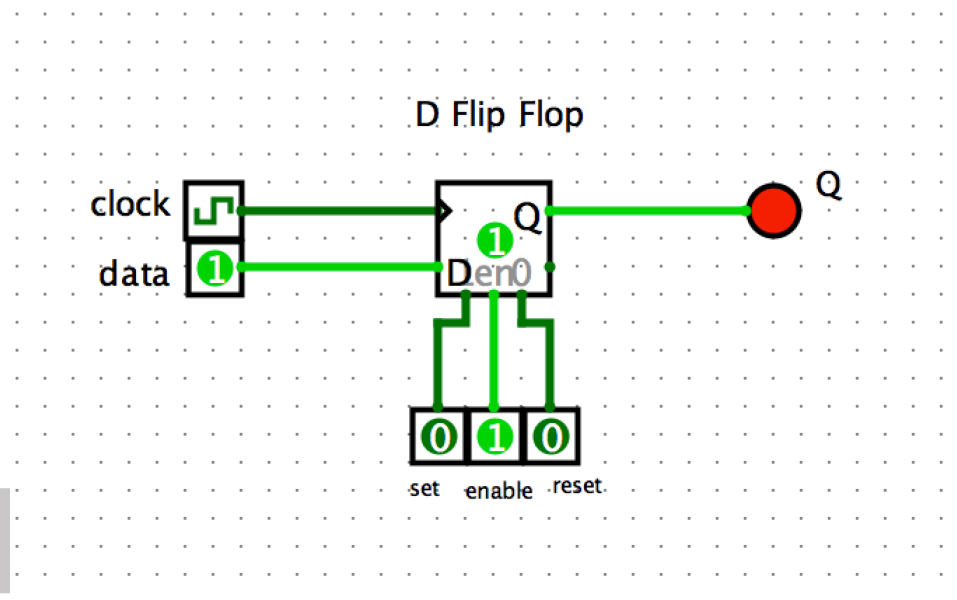- > Set data to high - Q goes high on next clock pulse. Stays high.
 - Set presets Q to high when pulled high
 - Reset clears Q when pulled high



D-TYPE FLIP-FLOP

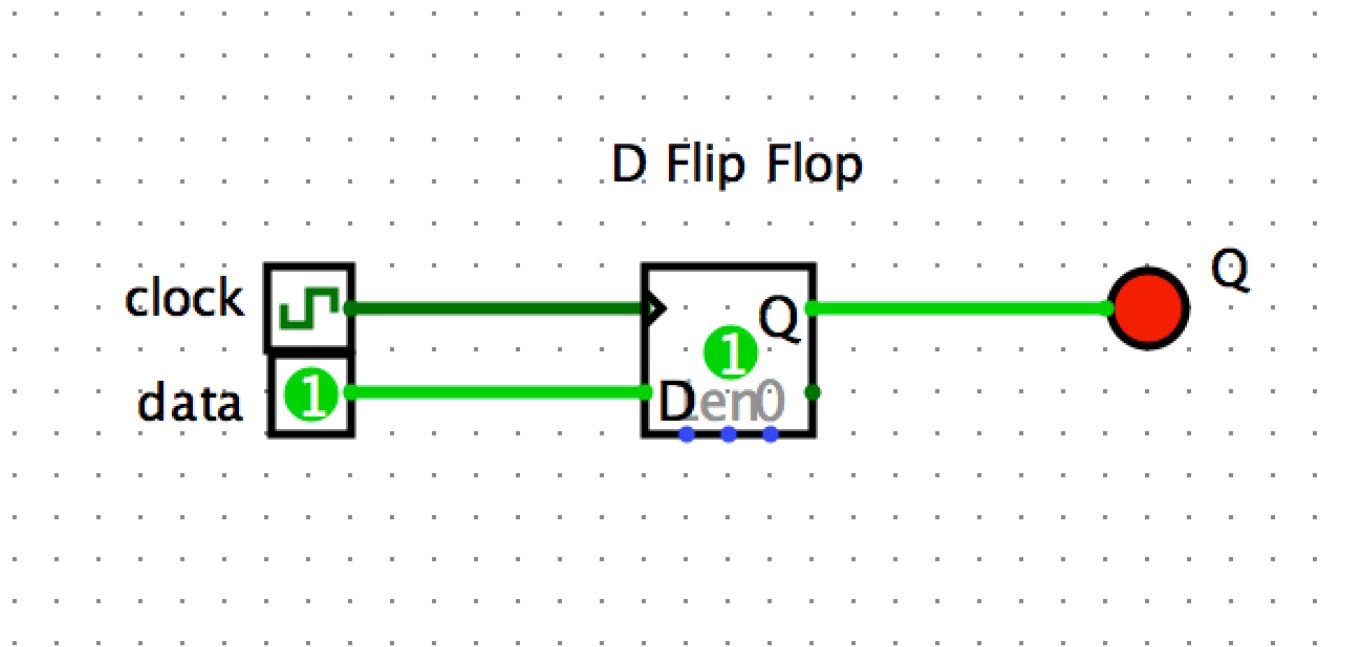- > In Logisim we can also leave PR' and CLR' disconnected.




D-FLIP-FLOPS AS A REGISTER OR LATCH

A register (many bits) or latch (usually one bit) can be made up from a series of D-Flip-Flops driven by a common clock.

The transfer from the D side to the Q side for all D flip flops occurs simultaneously as this clock changes.

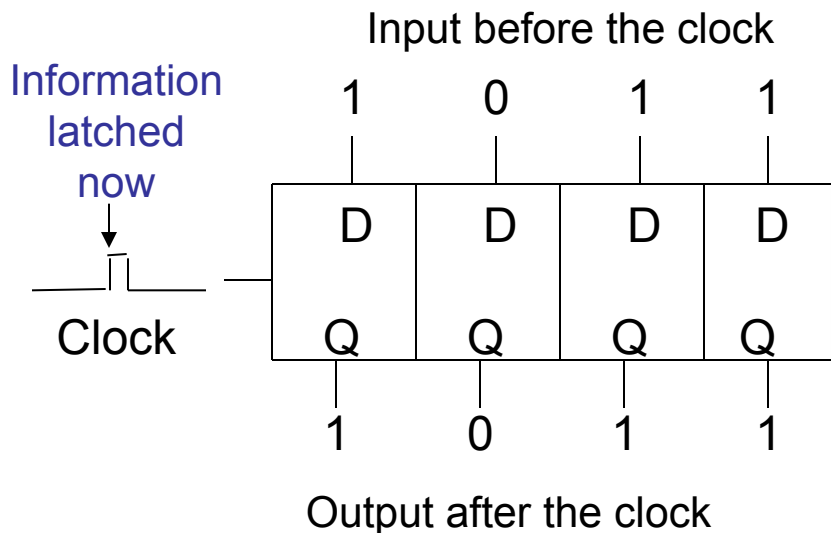
This arrangement is found in CPU registers



http://www.electronics-tutorials.ws/sequential/seq_4.html

8 BIT REGISTER

8 Bit Register

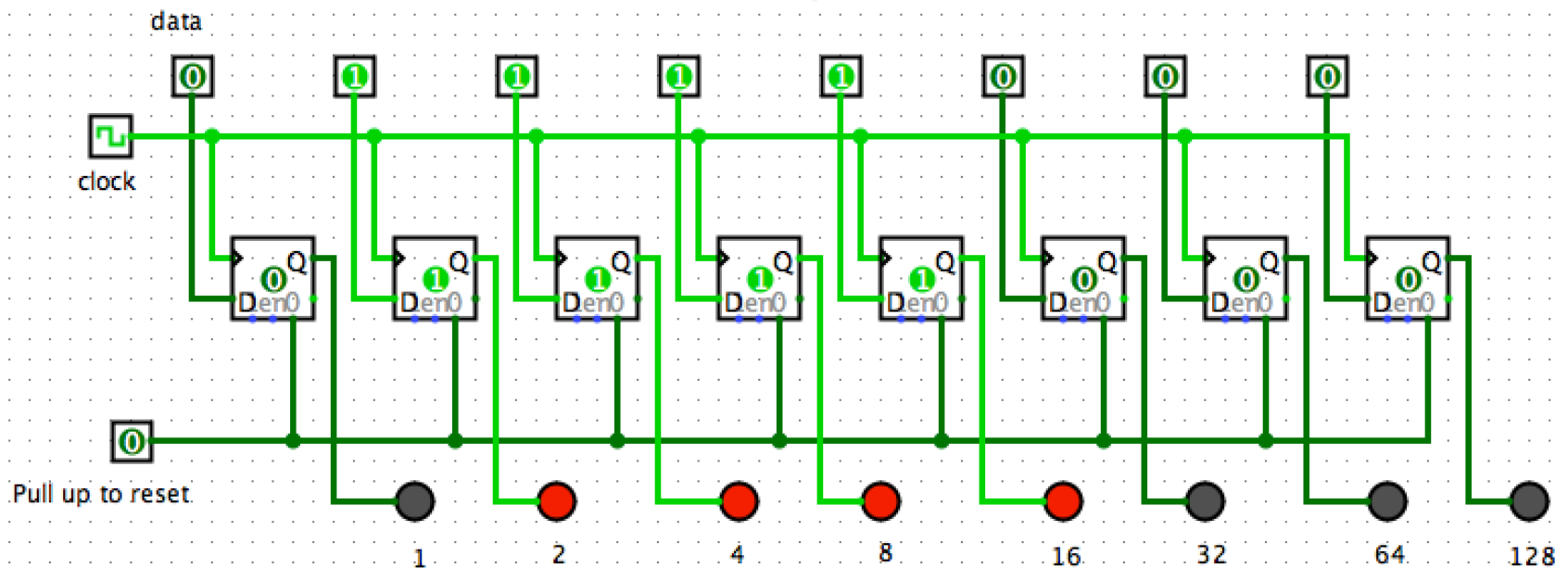

Little Endian

BIG ENDIAN AND LITTLE ENDIAN DATA FORMAT


- > Technical definition for the order of bytes:
 - Big Endian:
 - The most significant byte resides in the smallest memory address
 - Little Endian:
 - The least significant byte resides in the smallest memory address

BIT ENDIANNESS

- > Bits generally don't have an address, so definitions refer to the positional order of bits
- > Big Endian:
 - The most significant bit comes first
- > Little Endian:
 - The least significant bit comes first
- > This matters for interpreting the value of a bit string (especially if bits are received as a serial stream!)
 - Eg What is 1011 in decimal ?
 - 11_{10} (Big endian), or 13_{10} (Little endian)


8 BIT REGISTER

8 Bit Register

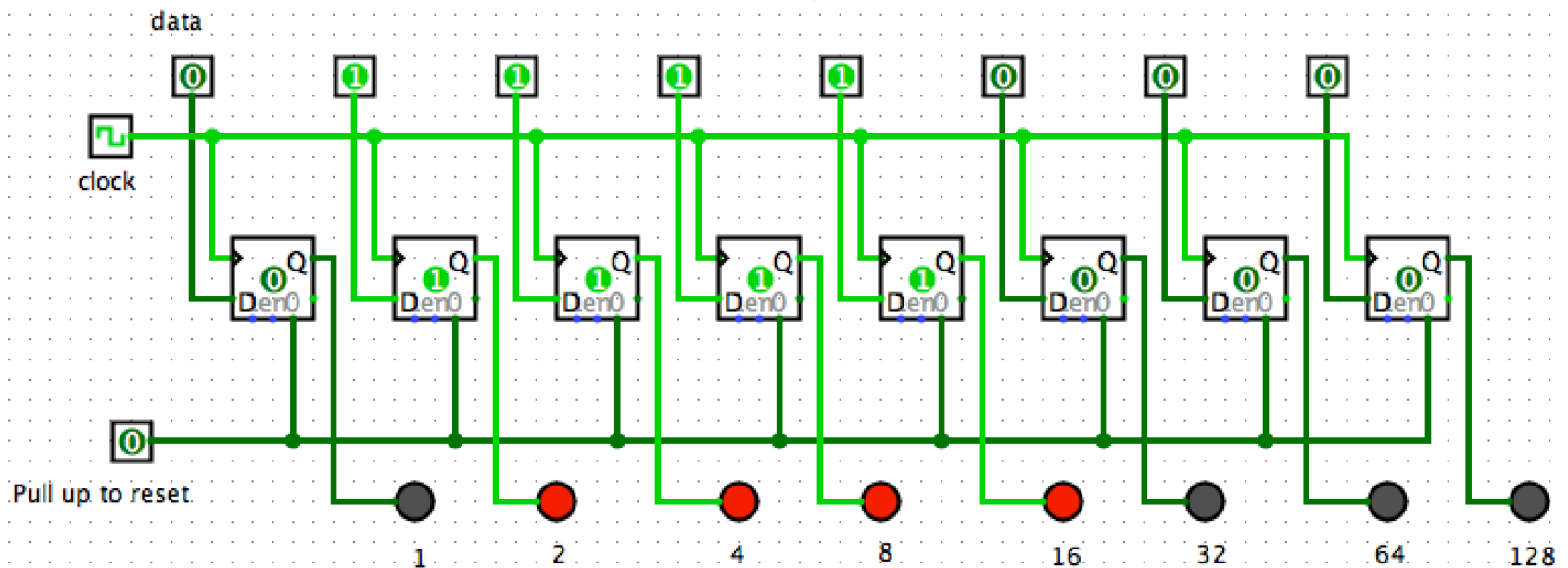

Little Endian

8 Bit Register

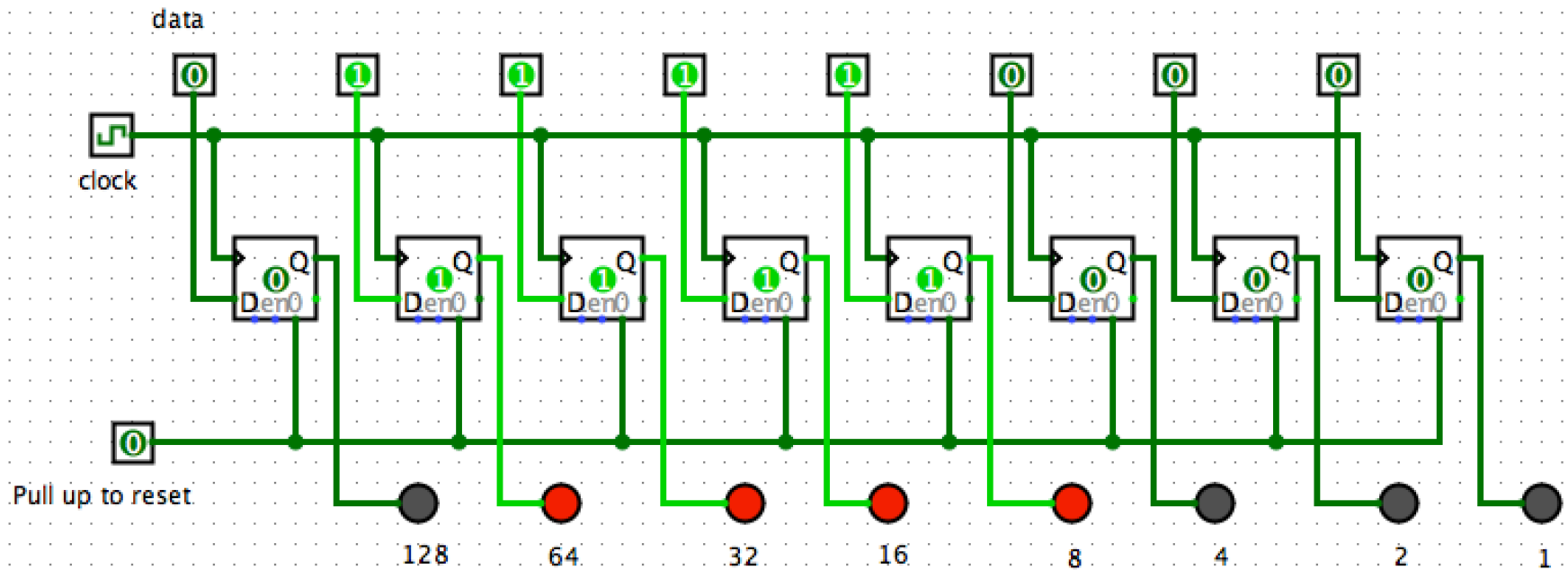

Big Endian

SUMMARY

- > D Flip Flops generally form the building blocks of registers
- > Registers:
 - Allow us to store bit strings that represent data
 - Reside close to the CPU, allowing fast and easy access
- > Bit Endianness determines how we interpret bit strings:
 - Big Endian: most significant bit comes first
 - Little Endian: least significant bit comes first
- > Next Lecture: ripple counters with JK Flip Flops