



SWINBURNE
UNIVERSITY OF
TECHNOLOGY

COS10004 Computer Systems

Lecture 1.6 Combinational Circuits - The Half Adder

CRICOS provider 00111D

Dr Chris McCarthy

COMBINATIONAL CIRCUIT

- > A combinational circuit is a connected arrangement of logic gates with the set of inputs and outputs.
- > A combinational circuit can be described by a truth table showing the binary relationship between n input variables and m output variables.
- > Two examples: half adder, full adder
- > These circuits serve as basic building blocks for the construction of more complicated arithmetic circuits.

BINARY ADDITION

> Consider:

0	1	0	1	1	1	0
+	0	0	1	1	1	0
	0	1	1	1	1	0
<hr/>						
1	0	0	1	0	1	0


carry ←

> We need 1-bit adders...

HALF-ADDER

- > The most basic arithmetic circuit is the addition of two binary digits.
- > A combinational circuit that performs the arithmetic addition of two bits is called a half-adder.
- > It consists of two inputs and two outputs:
 - Two inputs get summed
 - Two outputs: sum and carry bits
- > It is necessary to have two output bits because the sum $1 + 1$ is binary 10, which has two digits.

A half-adder

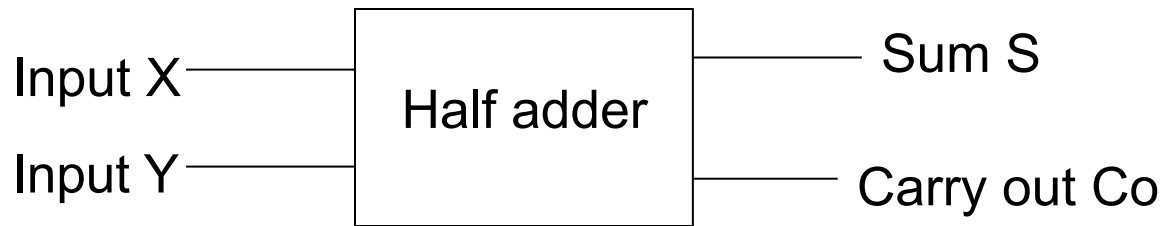


X	Y	S	Co
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = X \oplus Y$$

$$Co = X \cdot Y$$

The plus-circle
(modulo addition
of 1-bit values)
means XOR,
the dot
means AND


Half-adder

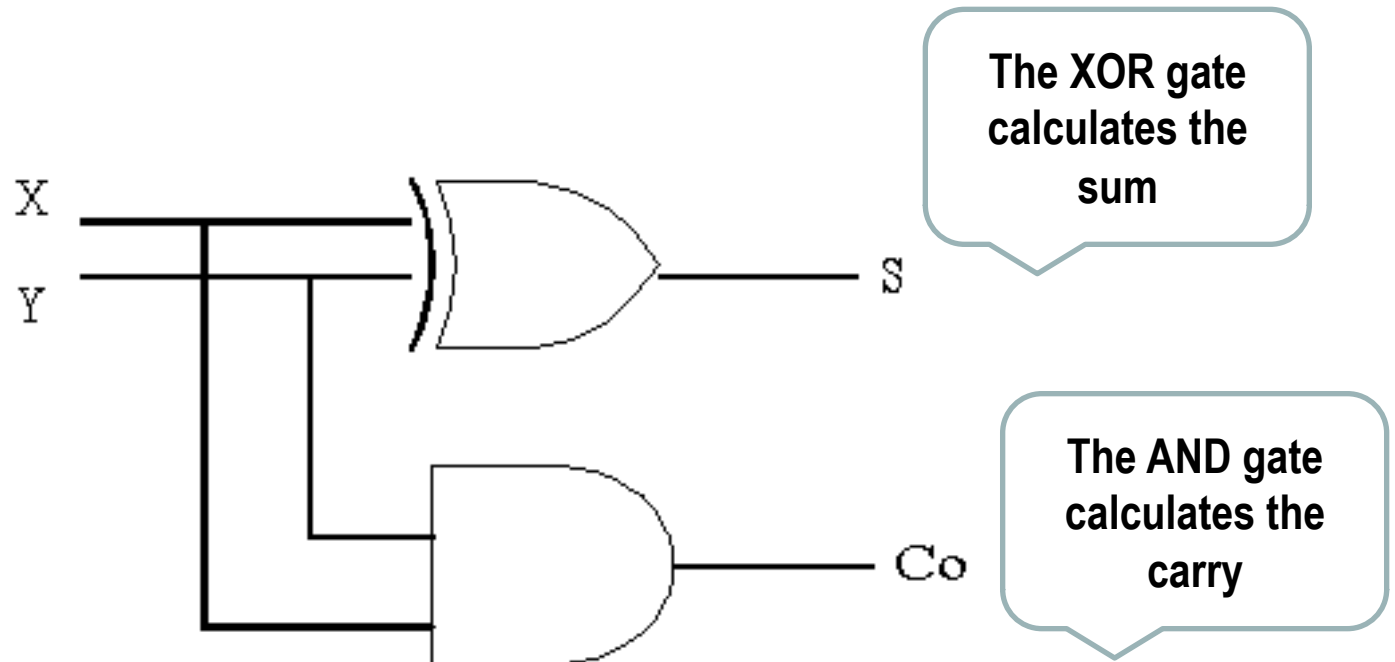

FULL-ADDER

- > A full-adder is a combination circuit that forms the arithmetic sum of three input bits.
- > It consists of **three inputs** and **two outputs**.
- > Two of the inputs represent the two bits to be added.
- > The **third input represents the carry** from the previous lower significant position.
- > **One of the outputs will be the carry** into the next higher significant position, i.e. into the next full adder.
 - Of course two output bits are necessary because the arithmetic sum of three binary digits ranges from 0 to 3, and 2 and 3 need two bits.


A full adder

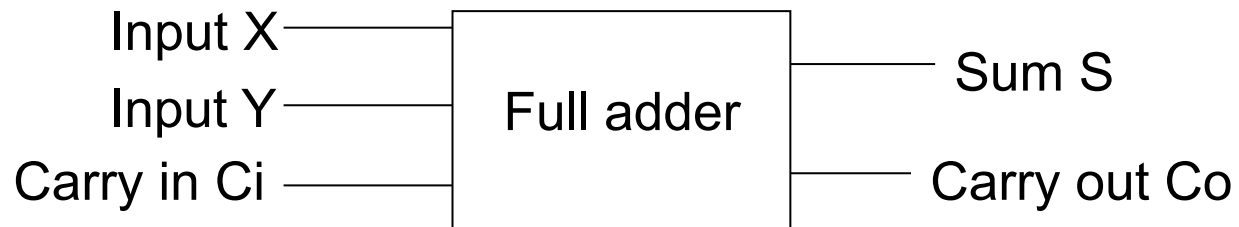

	Ci	X	Y	S			Co		
a	0	0	0	0	} $S = X \oplus Y$		0	} $Co = X \cdot Y$	
b	0	0	1	1			0		
c	0	1	0	1			0		
d	0	1	1	0			1		
e	1	0	0	1	} $S = \overline{X \oplus Y}$		0	} $Co = X + Y$	
f	1	0	1	0			1		
g	1	1	0	0			1		
h	1	1	1	1			1		

A full adder
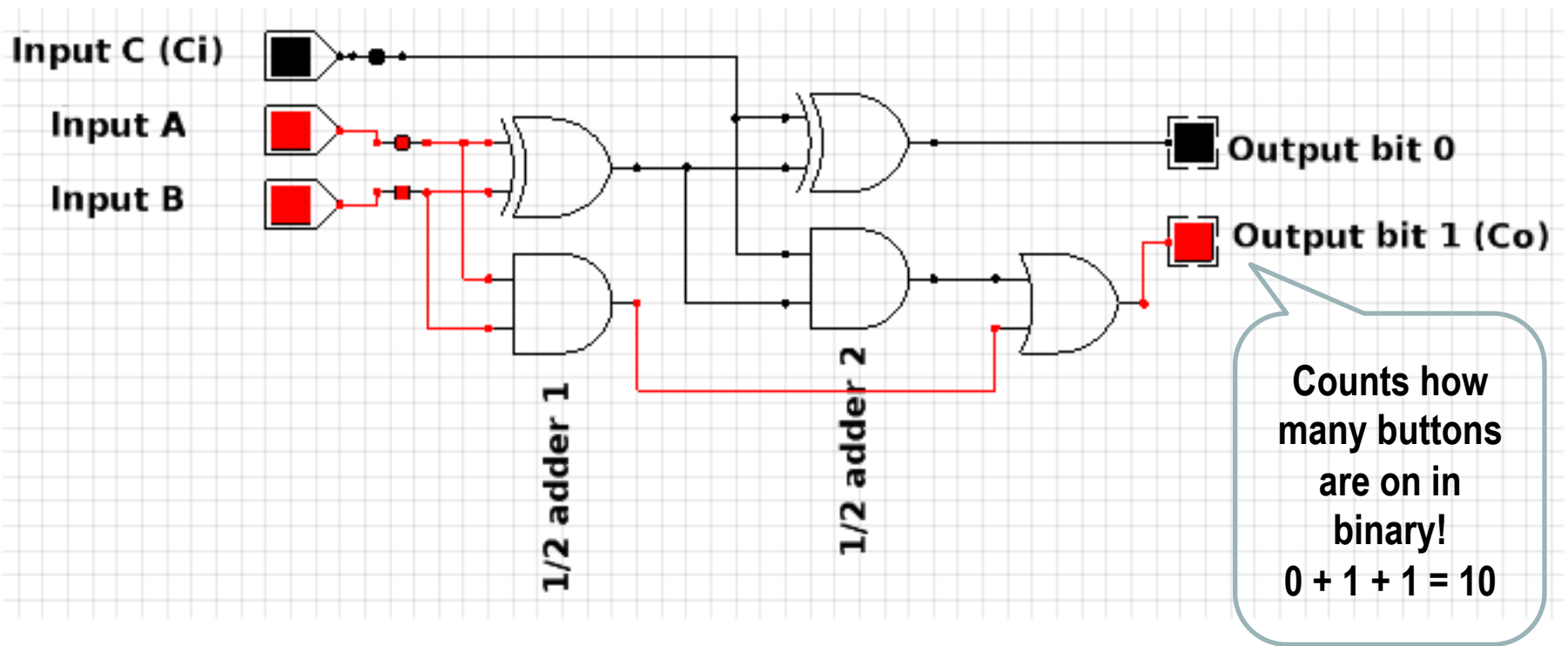
> We could make this from two half-adders:




Time to Imagine

- > A full-adder is a combination circuit that forms the arithmetic sum of three input bits.
- > Suppose we added a second full adder (A2) to the output of the first adder (A1), and connected the Ci pin of A2 to Co of A1?
- > Wouldn't we be able to add two 2-bit numbers?
- > A 3rd adder?
- > A 4th....



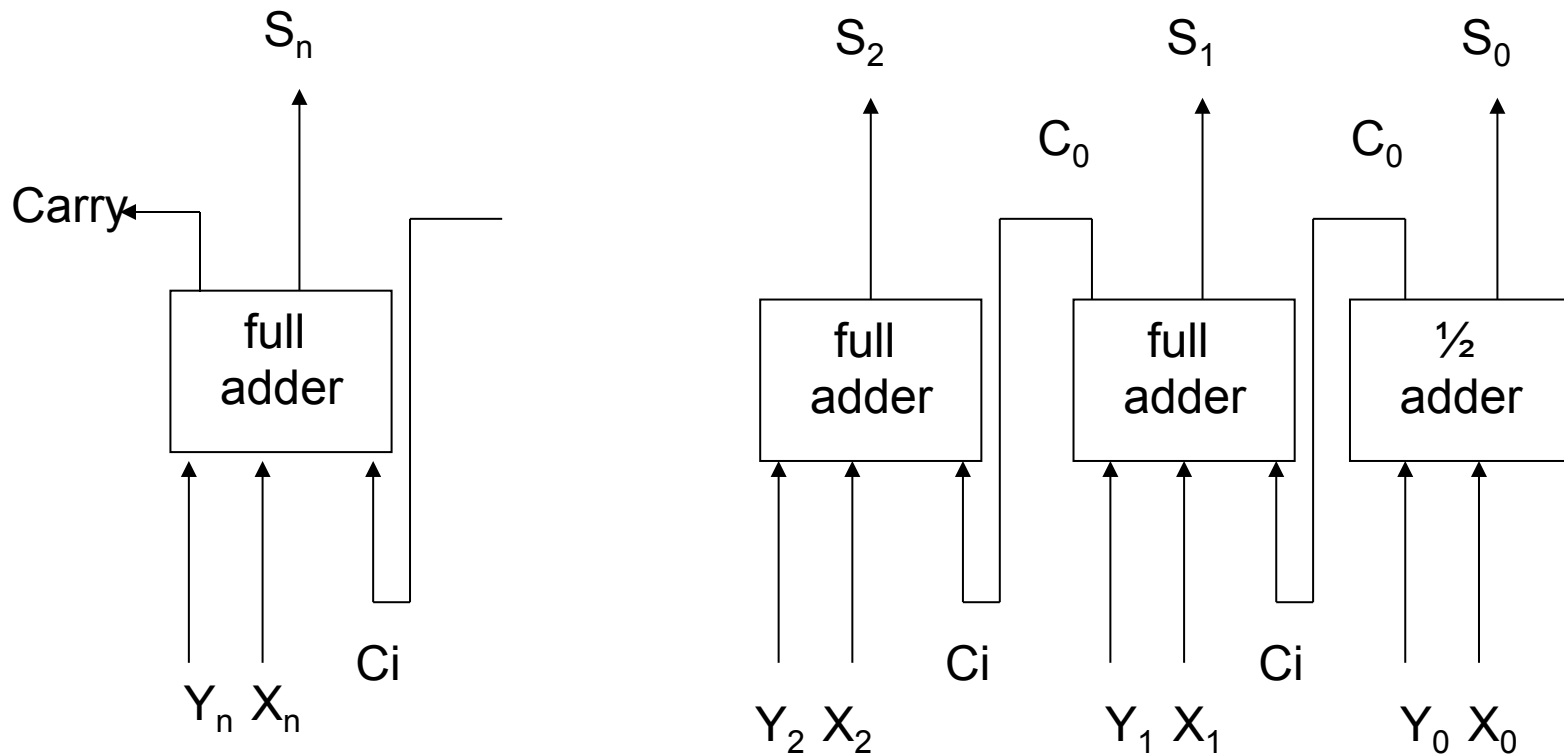Multi bit addition - combine 8 adders with carry to get 8-bit addition (of two 8-bit numbers).



In the Lab...

- > Play with Gates (in a “sim”) and construct truth tables.
- > Design a half adder
- > I made some video tutorials that might also help:
 - Logisim introduction: <https://youtu.be/fwPw28O5ORI>
 - Half-adder tutorial: <https://youtu.be/BpvlMgb40U4>
 - Full-adder tutorial: <https://youtu.be/1qLAk0AsH40>



Summary of Week 1

- > Computer Systems:
 - We're building a computer up conceptually!
 - Get your Pi and hardware
 - Check Canvas regularly
- > Information and bits
- > Digital Circuit Design:
 - Gates, Half-Adders and Full-Adders
- > Next week: more complex circuits and Flip Flops (memory)!

