



SWINBURNE  
UNIVERSITY OF  
TECHNOLOGY

# **COS10004 Computer Systems**

## **Lecture 4.3: Let's build a stack!**

CRICOS provider 00111D

*Dr Chris McCarthy*





# STACKS

---

- > Random access memory requires knowing the address of every byte/word you want to access
- > Hardware stacks created out of dedicated shift registers
- > So let's build one!

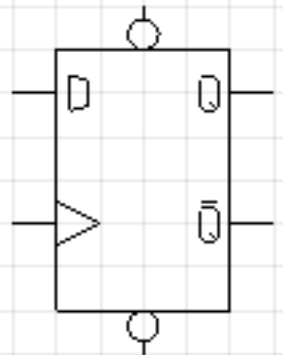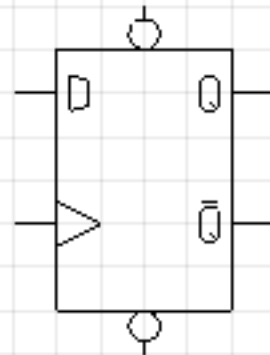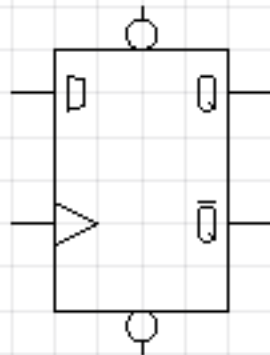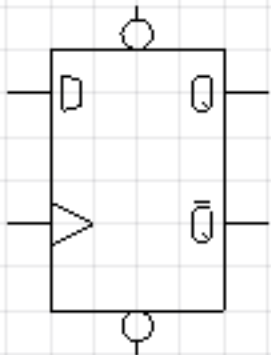
# LET'S BUILD A STACK...

- > Start with a bi-directional shift register...
- > 1. Start off with 4 D flip-flops:




## 2. ADD THE STANDARD SIGNALS

> Clock

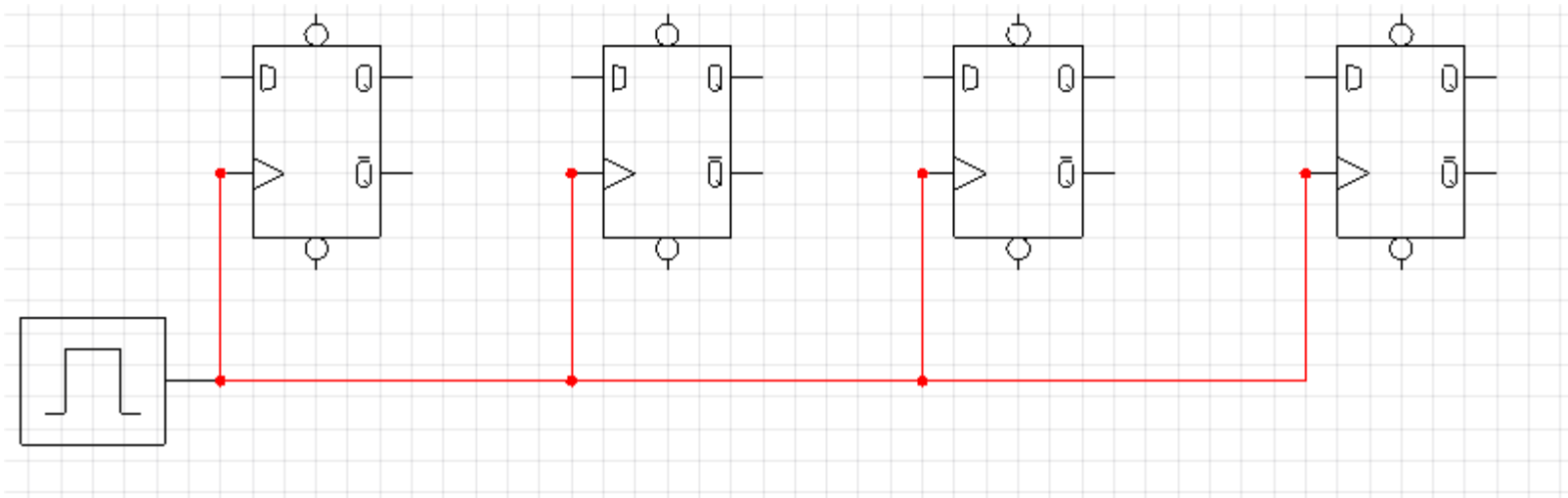

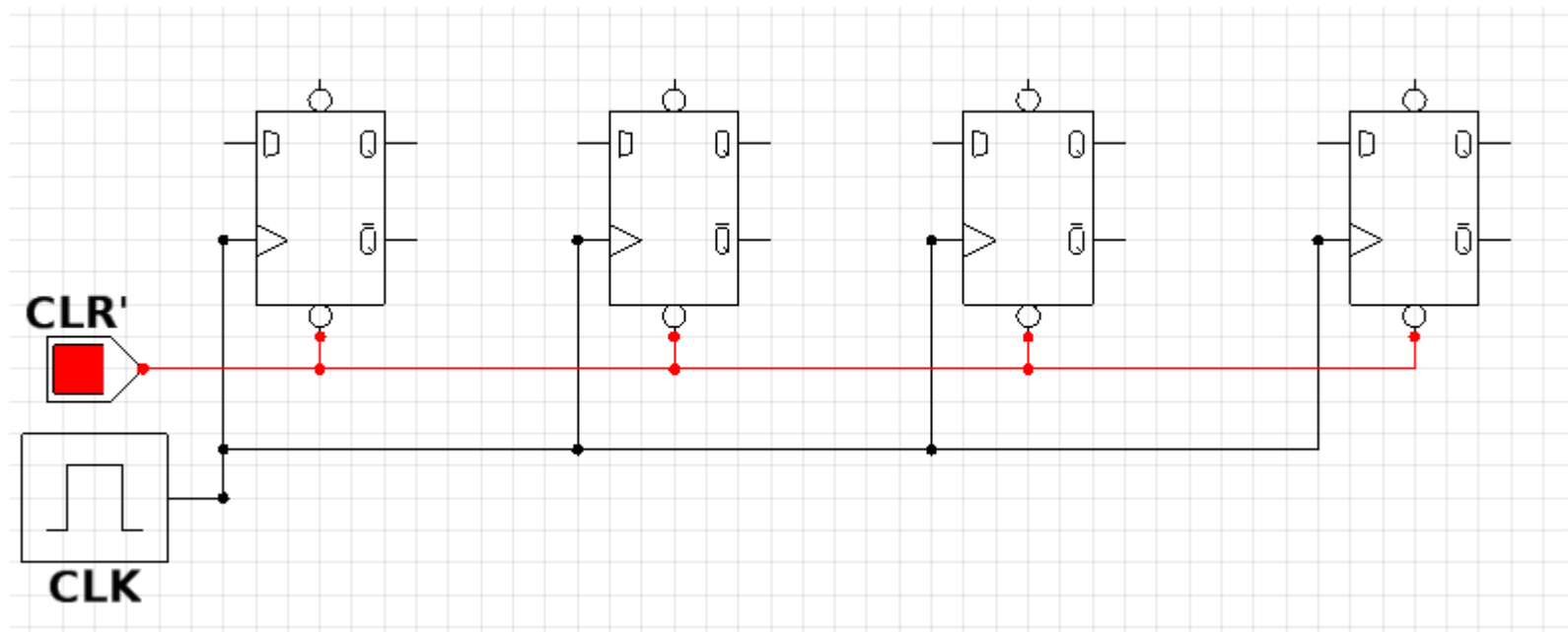
> CLR (resets flip flops when up in Logisim)




# ADD THE SERIAL INPUT (D)

> Data is the serial input (SI)

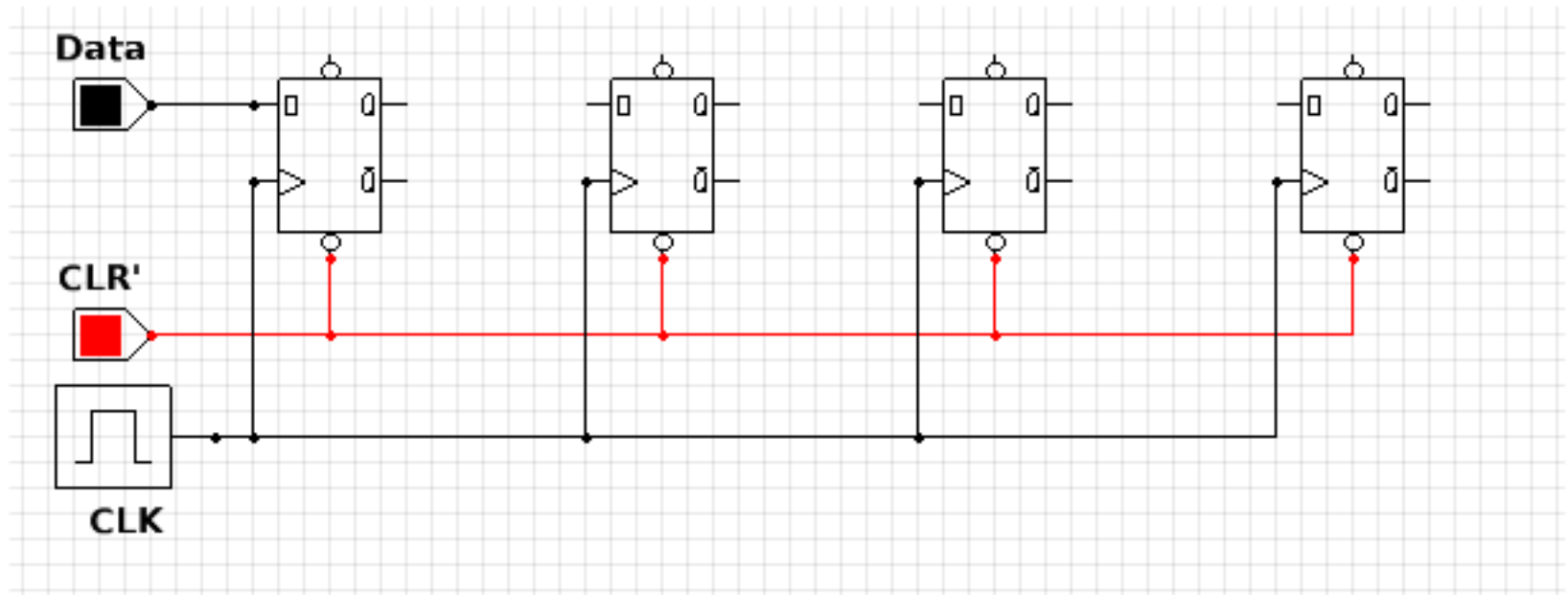

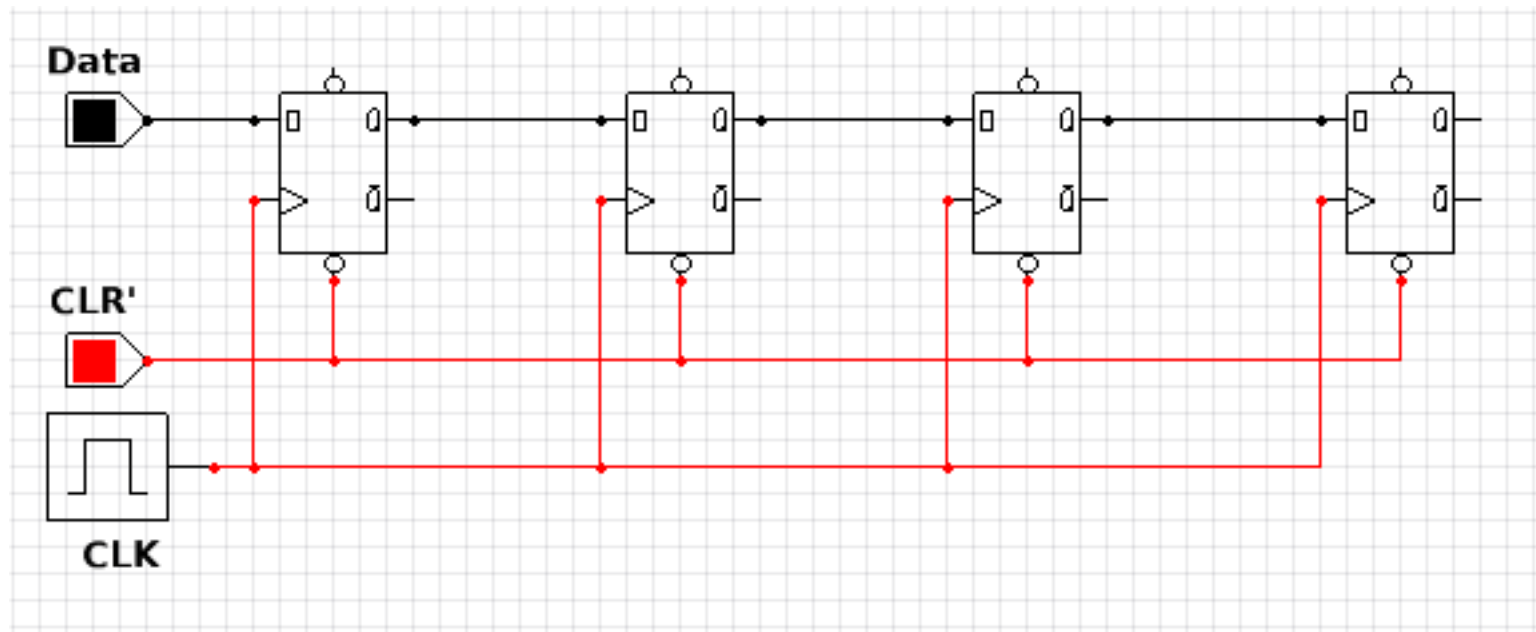
# CONNECT EACH Q OUTPUT TO THE NEXT DATA INPUT


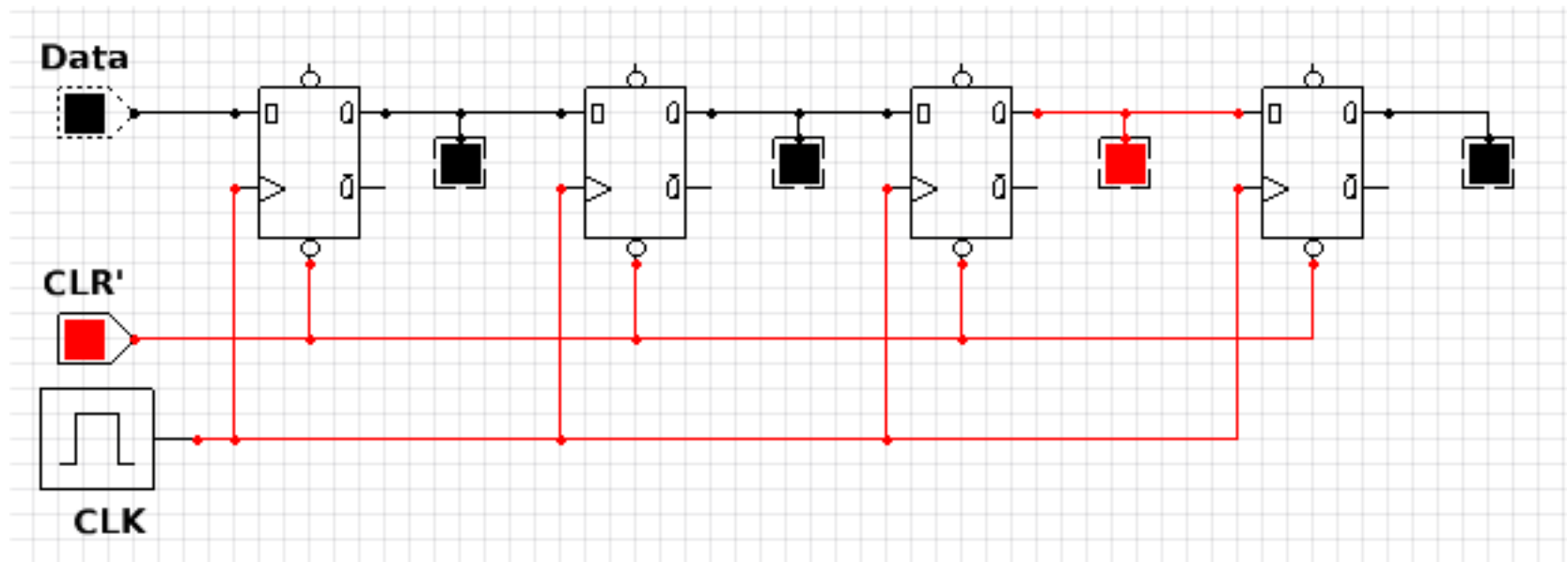
# ADD SOME LEDs TO SEE THE PARALLEL OUTPUT / REGISTER STATE


- > We can now modulate the Data input and see the **on** state propagate through the register (left to right).




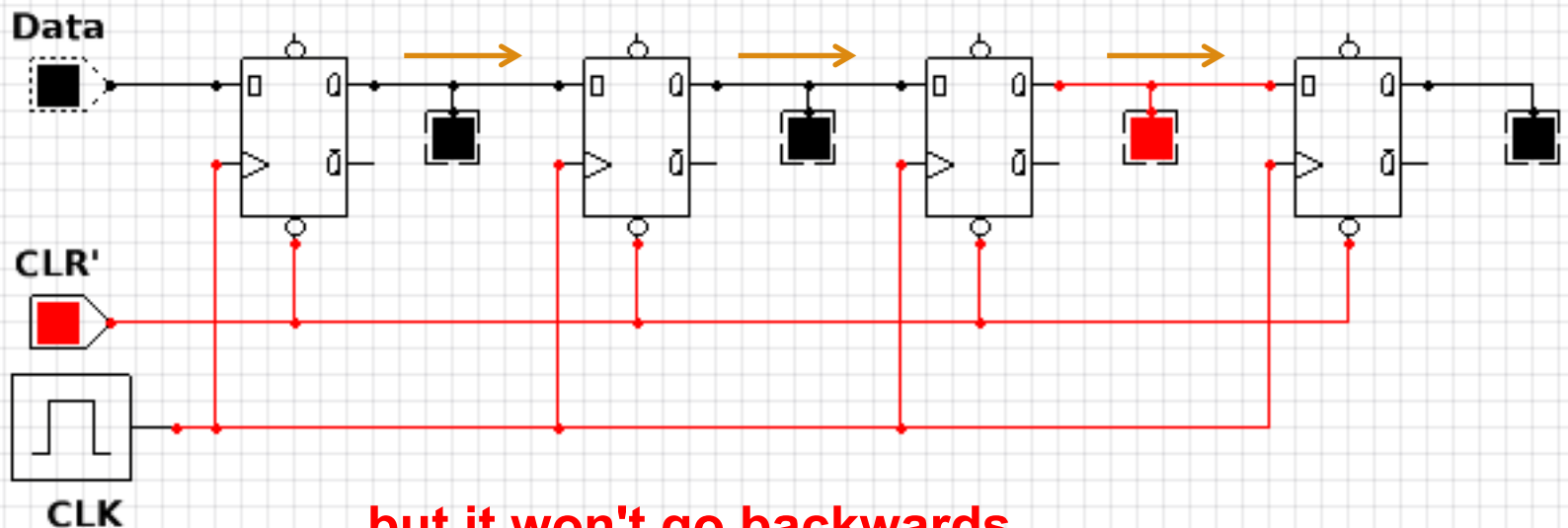
## THIS CIRCUIT WILL DO MOST THINGS WE NEED:


- > To get serial out, record the state of the right-most LED.
- > To get parallel out, feed each LED into a register (latch) and stop the clock when the conversion is complete.
- > To do parallel input, OR each D input with the state of a register and start the clock.



**but it won't go backwards...**
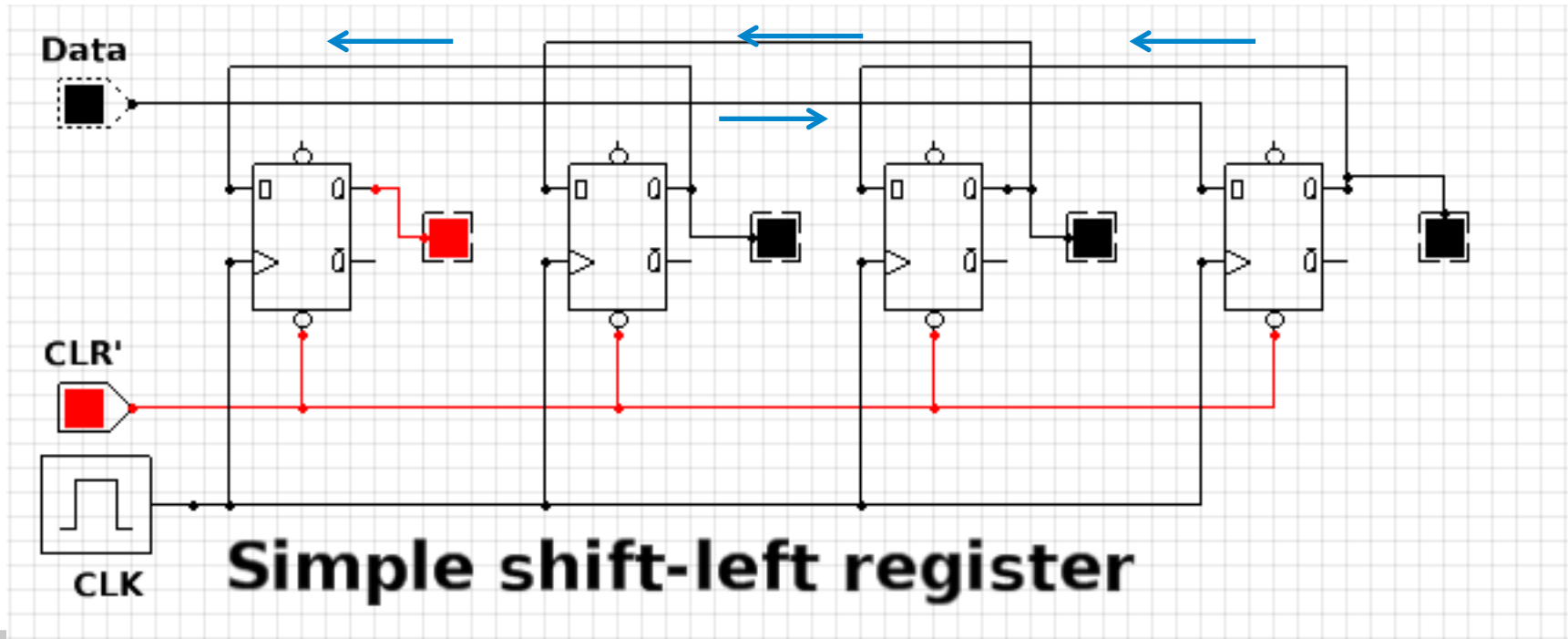
# HOW DO WE MAKE IT GO BACKWARDS?

- > Wire-up the cascade backwards
- > Data goes in the far end, each Q outputs to the D input of the previous Flip-Flop.






# HOW DO WE MAKE THE DIRECTION SELECTABLE?

---

- > More specifically, we need to determine from which direction each Flip Flop will receive its input.
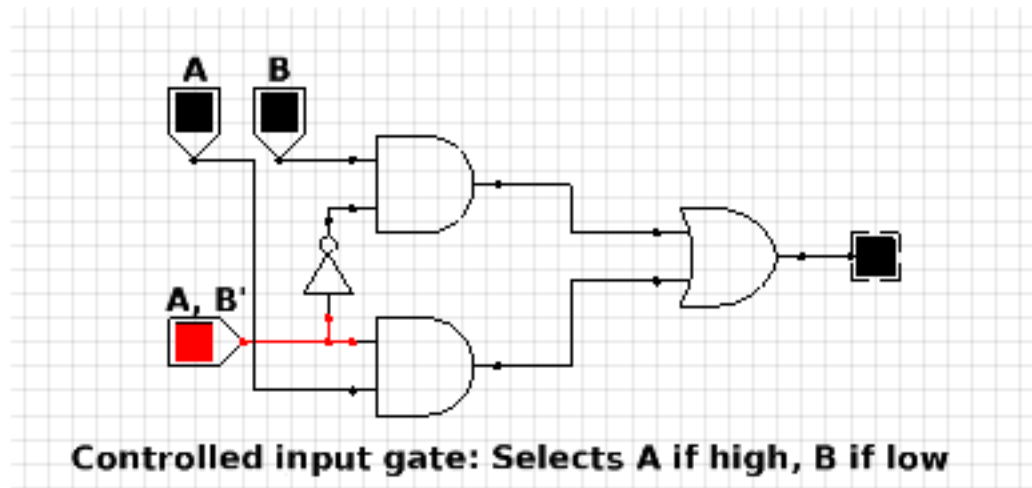
# HOW DO WE MAKE THE DIRECTION SELECTABLE?


- > A controlled gate (remember Week 2!).



# PROGRAMMABLE WIRING

- > We can use one of these circuits for each input to a Flip-Flop, and use a common control signal to determine direction.


A, B'	Output
1	A
0	B

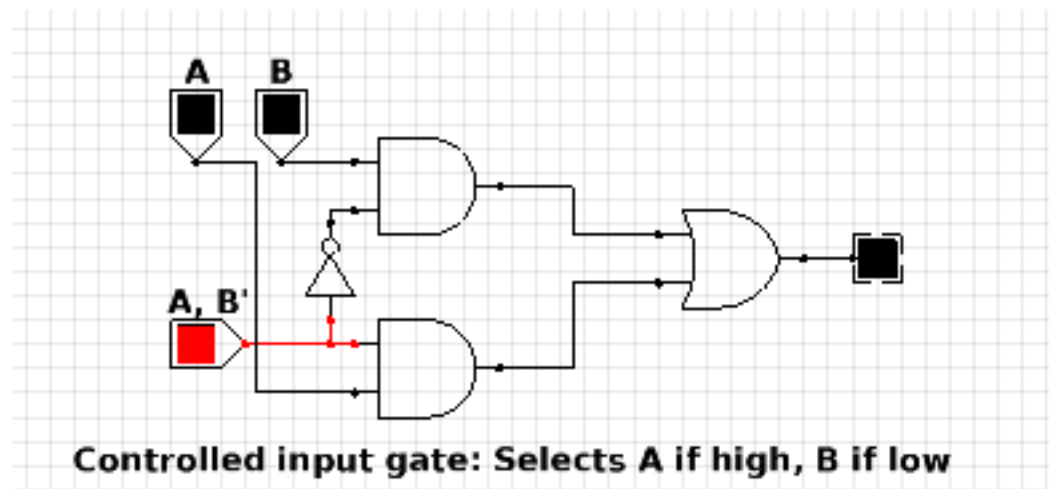

## SELECTING THE OUTPUT WITH GATES

- > We also need to determine which direction output from a Flip Flop flows!
- > This circuit has a common input, and selectable output.
- > We can use one of these for each output from a Flip-Flop, and use a common control signal to determine direction.

A, B'	Input
1	A
0	B

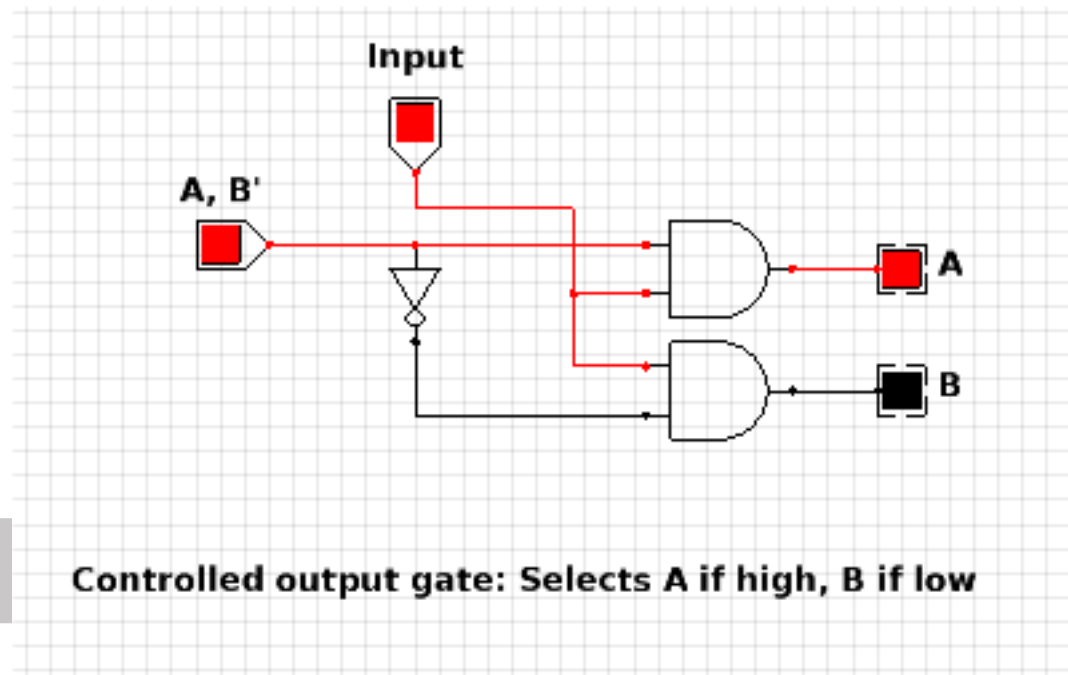


# LET'S PUT THIS ALL TOGETHER (JUST 2 FFs TO START WITH)

L', R



Data

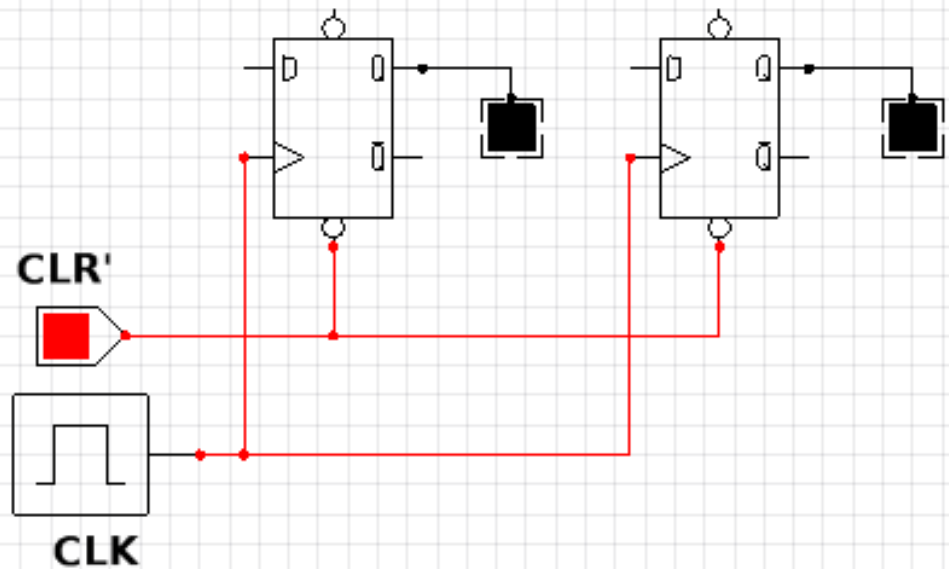






# ADD THE GATES FOR SETTING INPUT


L', R



Data

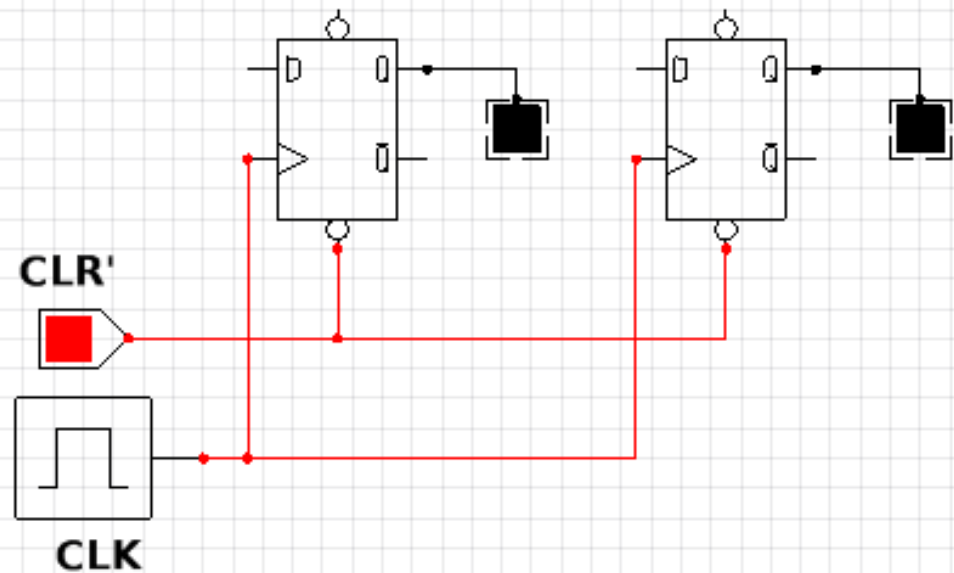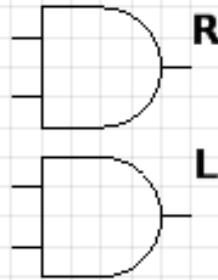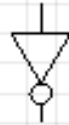


## SELECT INPUT

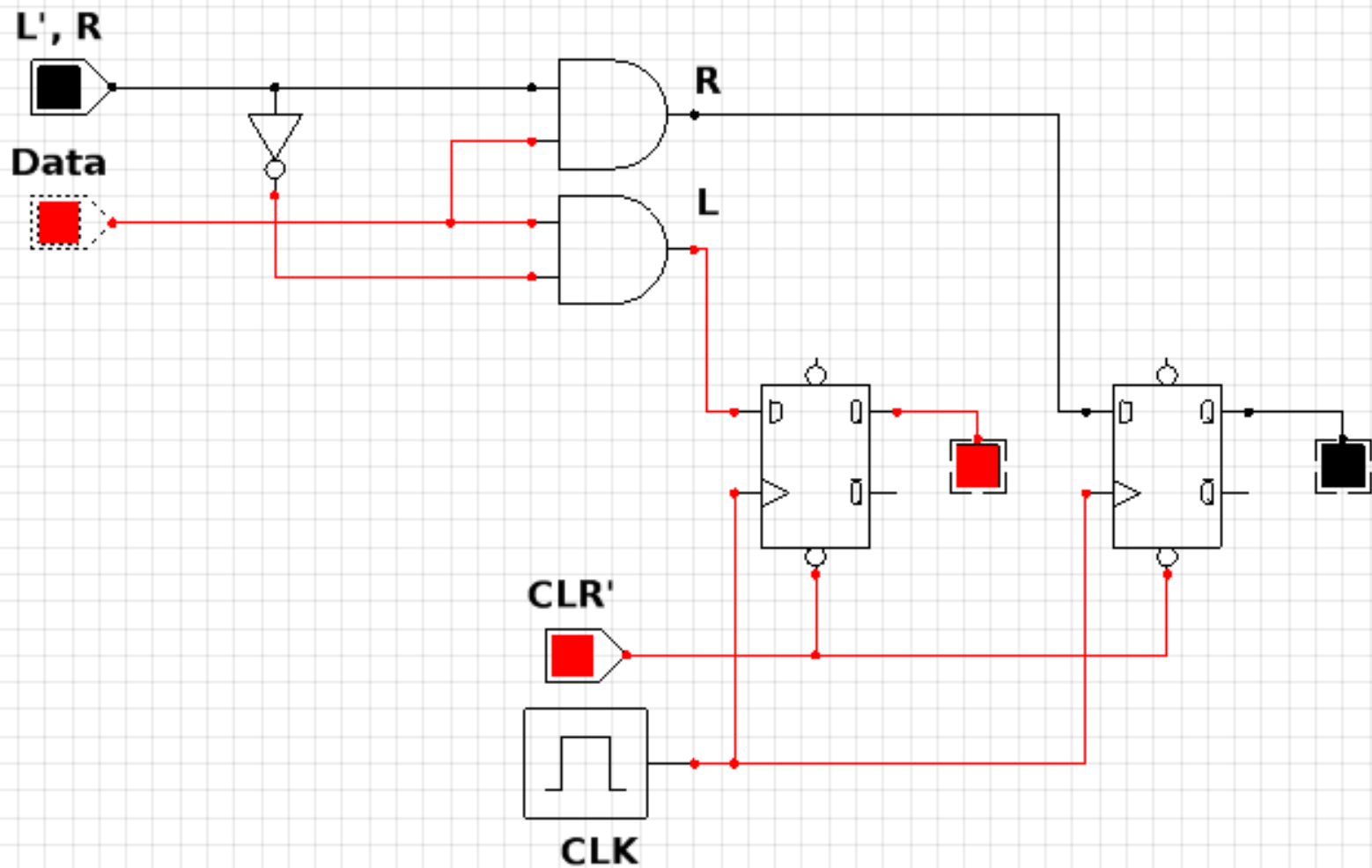


# ADD THE OUTPUT DIRECTION SELECTION

> R circuit enabled (red)

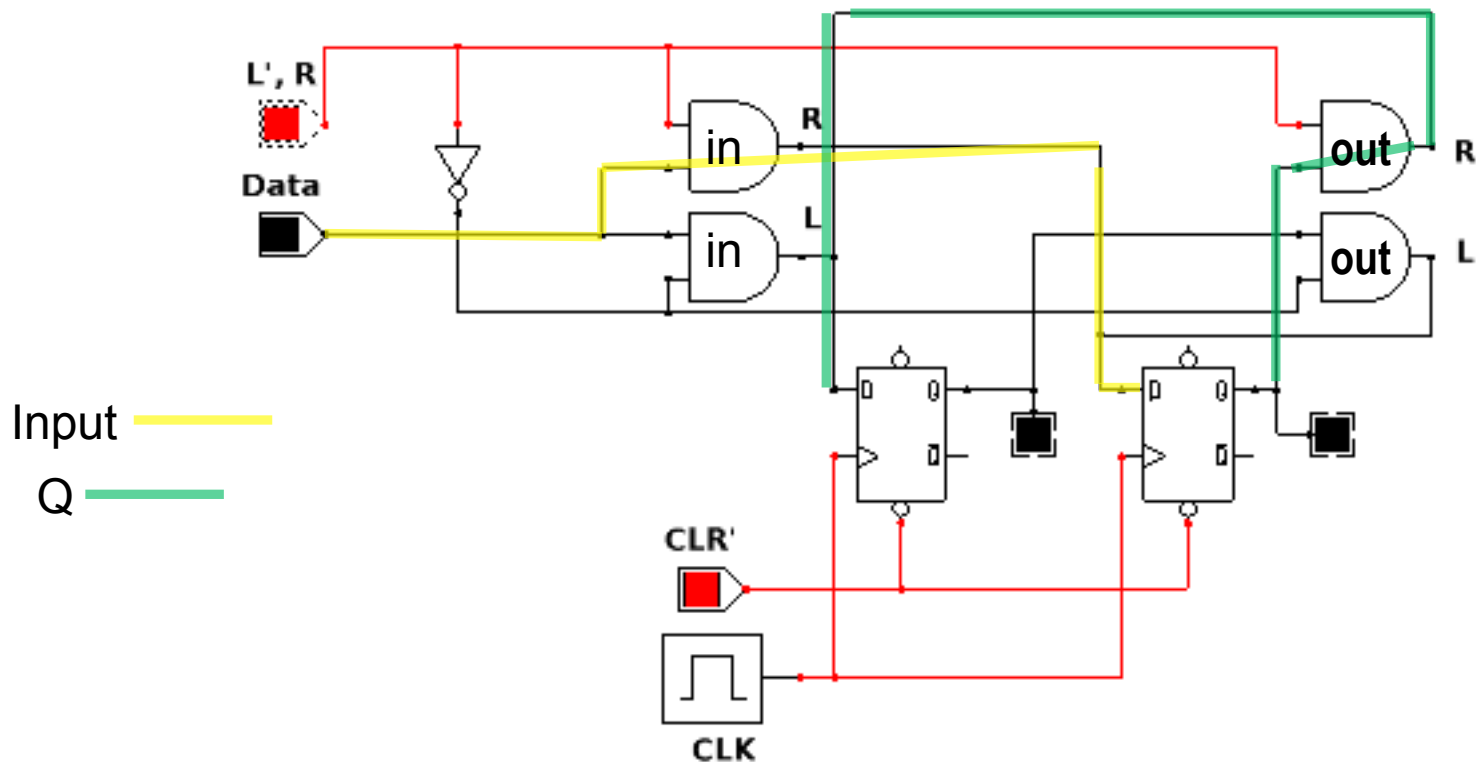


# OTHER DIRECTION SELECTED?

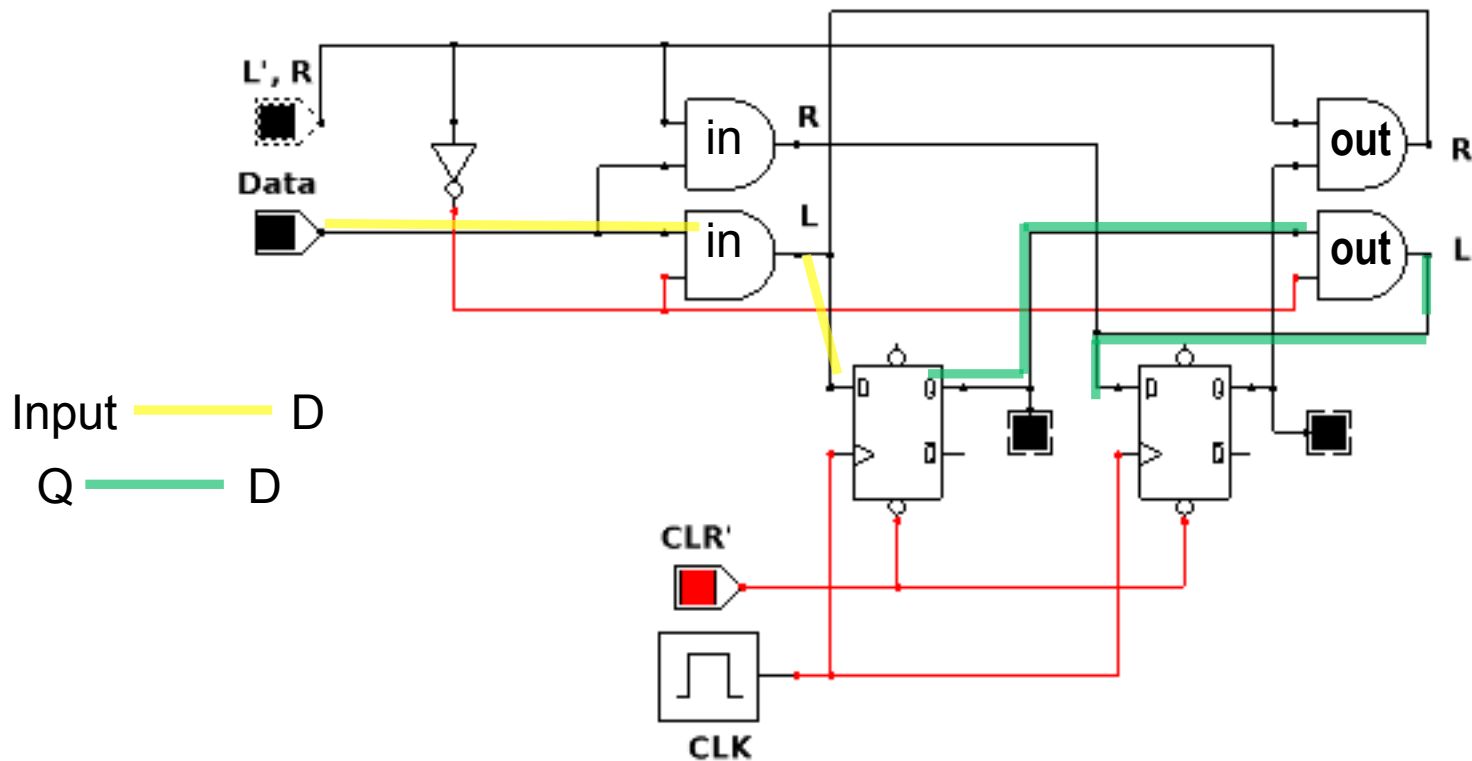

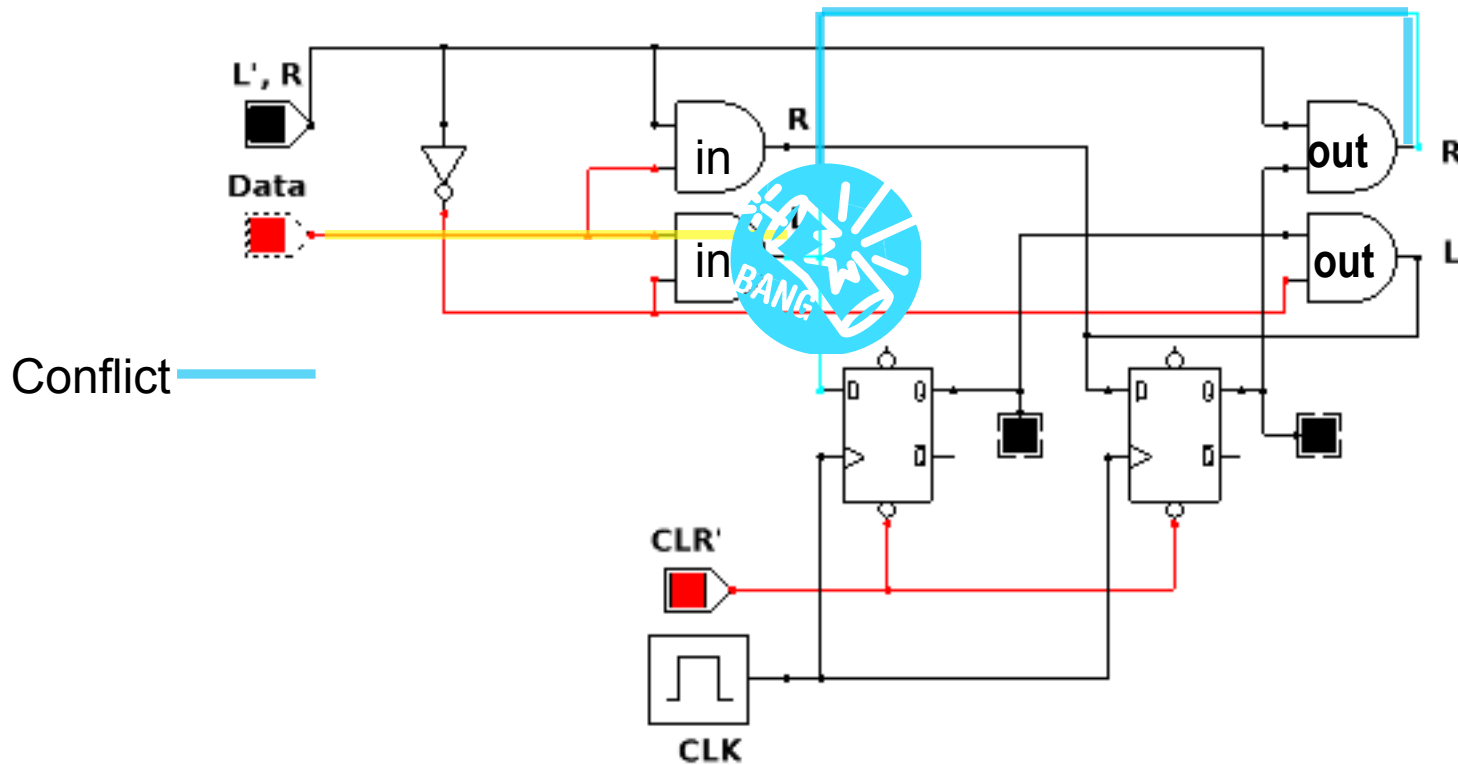
# WHAT COULD POSSIBLY GO WRONG?

- > Can't **short the outputs** of two gates together.
- > Have to **Add** with an **OR** gate.


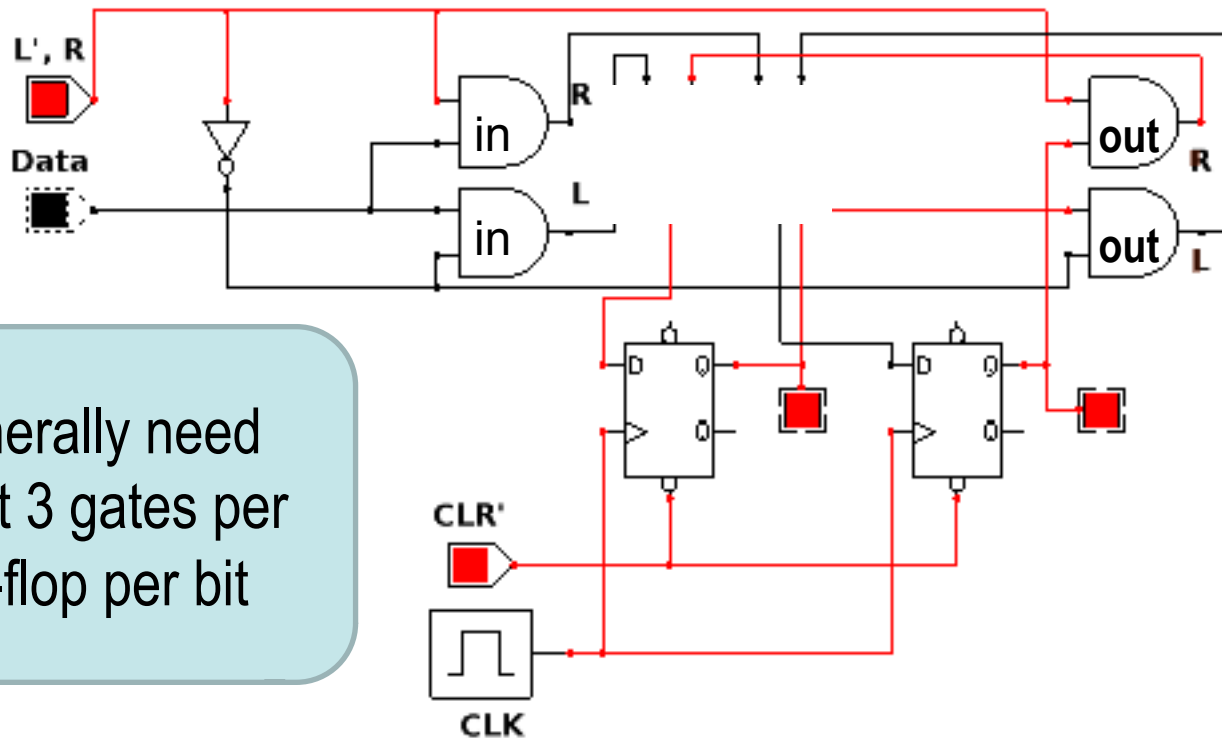
## THE FIX


- > The OR gates combine the outputs of the controlling AND gates and pass through the signal from whichever one is enabled... to the D inputs on each Flip-Flop.



Generally need  
about 3 gates per  
flip-flop per bit
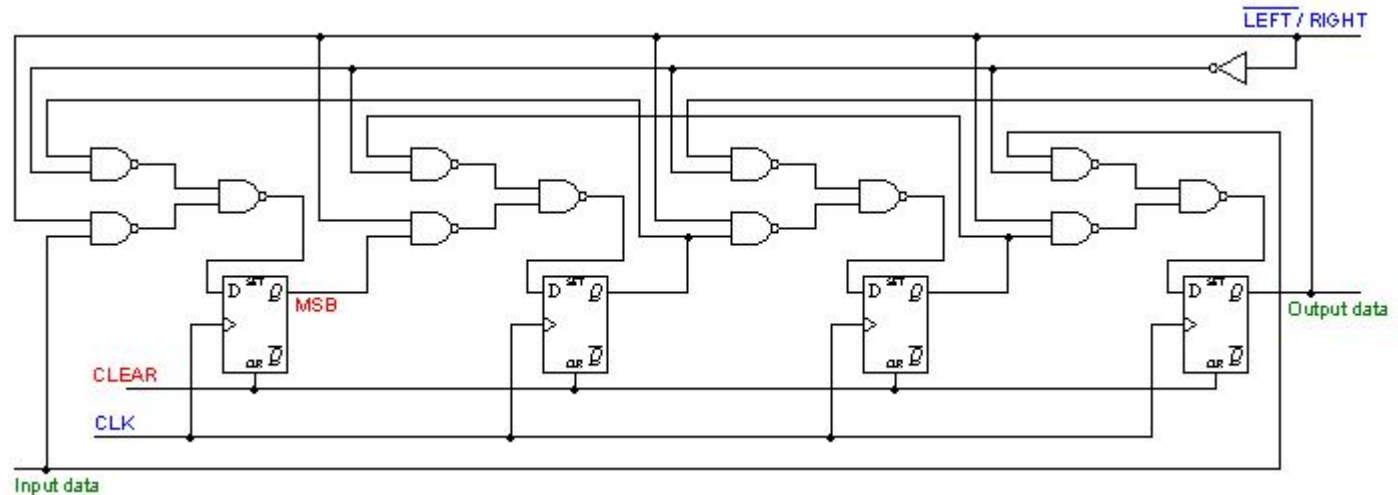
# NEED MORE DEPTH?

- > This is a 4-deep shift register ([http://www.ee.usyd.edu.au/tutorials/digital\\_tutorial/part2/register06.html](http://www.ee.usyd.edu.au/tutorials/digital_tutorial/part2/register06.html)).
- > As you can see, there are alternative ways of wiring it up, with different logic gates.



## TO MAKE A STACK...

- > So far we have made a 2-stage bi-directional 1-bit shift register.
- > To make a proper stack:
  1. Add depth (flip-flops with associated control logic)
  2. Add width (bits) in parallel (common clock, control signals).
    - identical shift-registers - one for each bit.



# SUMMARY

---

- > Hardware stacks formed using banks of shift registers
- > Simple input selective circuits allow direction selectability:
  - Programmable gates !
- > To make a proper stack:
  1. Add depth (flip-flops with associated control logic)
  2. Add width (bits) in parallel (common clock, control signals).
    - identical shift-registers - one for each bit.