

COS10004 Computer Systems


Lecture 3.3: More ripple counters

CRICOS provider 00111D


Dr Chris McCarthy

RIPPLE COUNTER

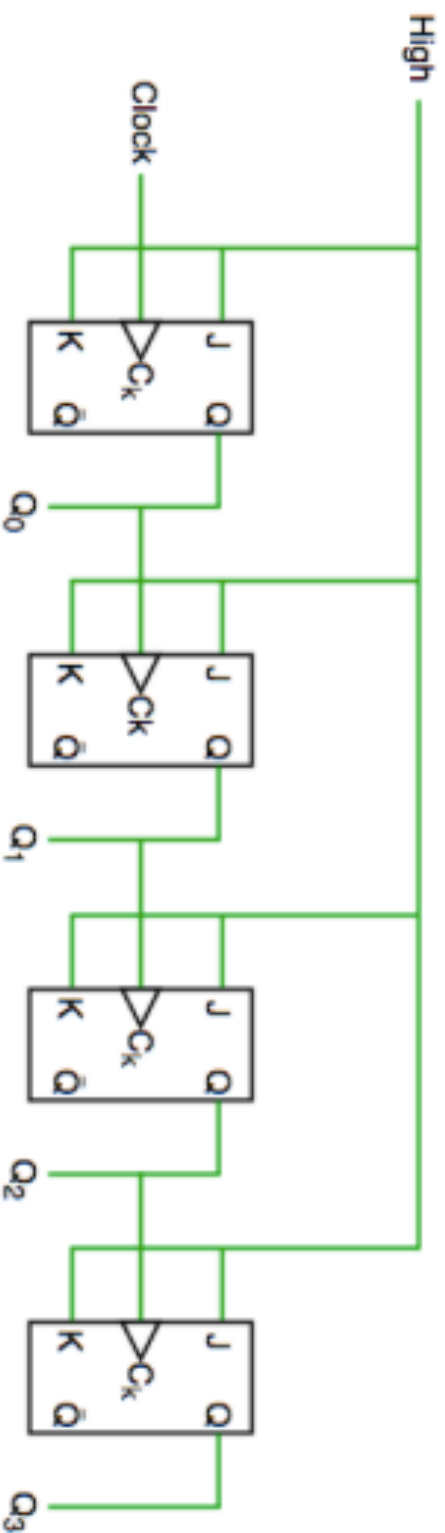- > Ripple counters utilise the toggle setting of J-K Flip Flops:



RIPPLE COUNTER

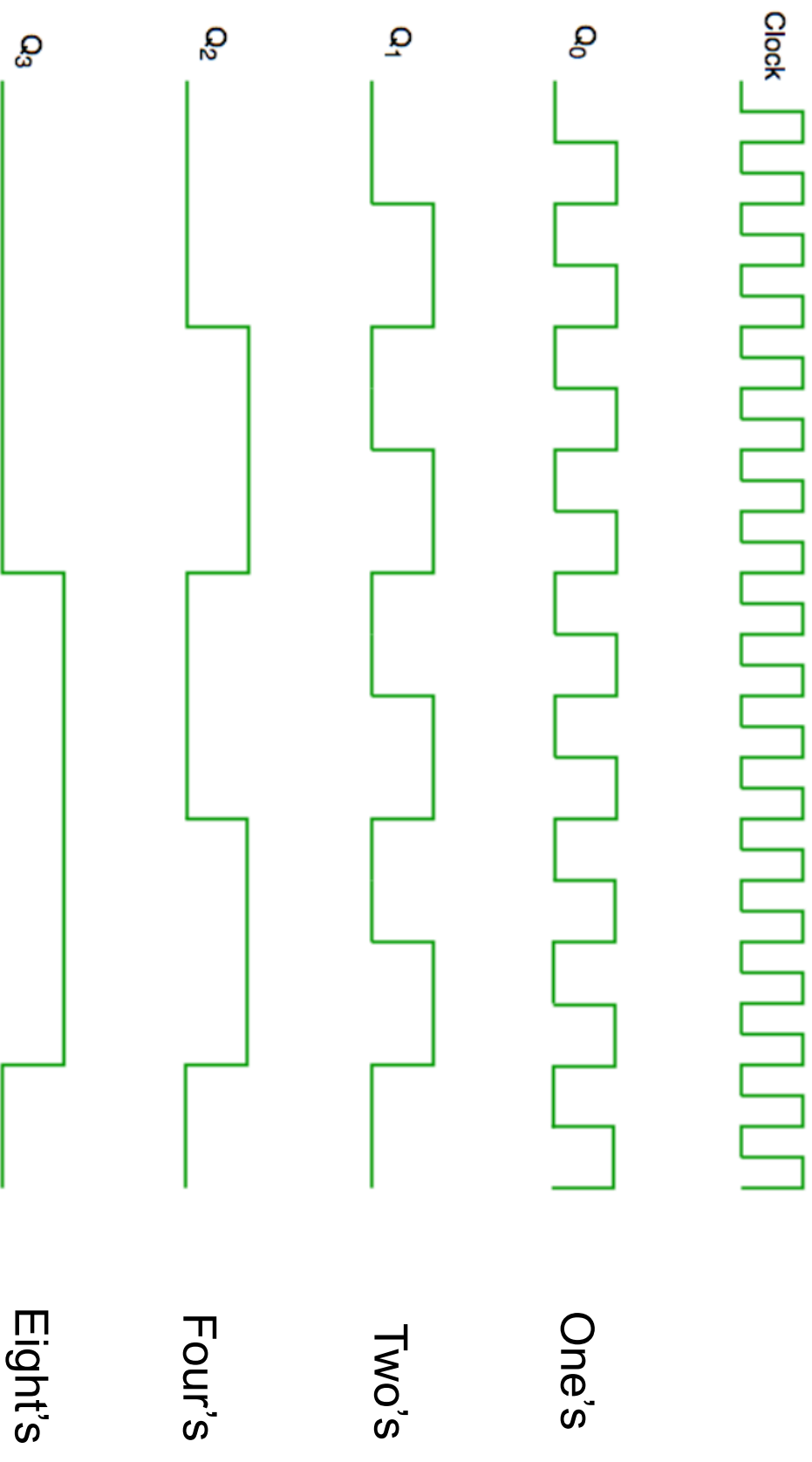

MORE COUNTERS

- > Suppose we want to count up to a power of two? For example 6
- > Why 6 you ask ?

MORE COUNTERS

- > Suppose we want to count in a modulo that is not a neat power of two? For example 6
- > Why 6 you ask ?



MOD 6 COUNTER

- What do we need to do?
 - An incrementing counter
 - A forced reset of all Flip Flops to zero when the counter reaches 6

MODULO 6 COUNTER

> What do we need to do ?

- An incrementing counter:

falling edge trigger – easy!

- A forced reset of all Flip Flops to zero when the counter reaches 6:

some extra logic gates to monitor things, and trigger a FF reset - not too tricky


MODULO 6 COUNTER

- Have a go !
 - Detect the illegal state (6)
 - Reset the FFs to wrap around to zero

MODULO 6 COUNTER WITH A MOMENTARY ILLEGAL STATE

- Detecting the first illegal state (6 in this case) and immediately resetting to 0 (don't wait for the clock) by using the asynchronous master reset (MR) or CLR'

- This circuit uses a *cascading clock*

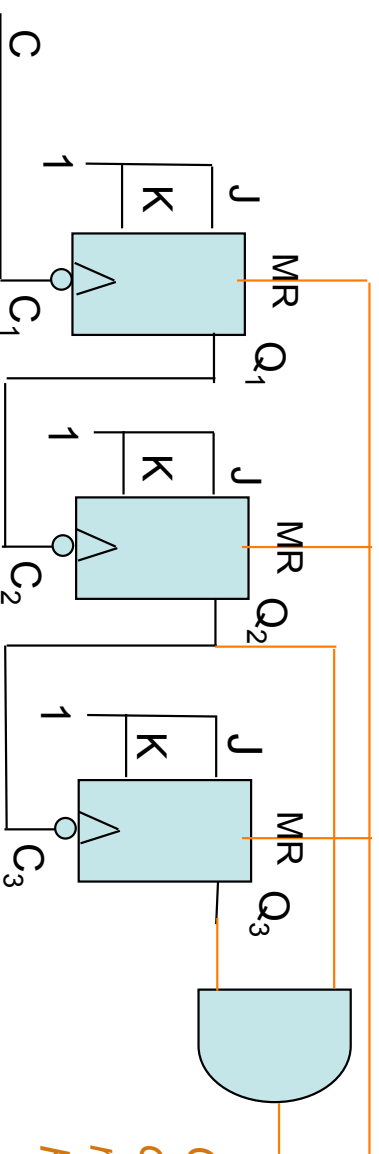

Goes 1 if counter on 6 or 7 forcing the master resets to clear each F/ F to zero

SUMMARY

- Counters don't have to wrap around at powers of 2
- Can use outputs of FFs and appropriate logic gates to detect "illegal state"
- Slight problem though:
 - Master reset is asynchronous
 - The illegal state momentarily still happens !
 - We can do better !in fact .. We NEED to do better
....next lecture