



SWINBURNE  
UNIVERSITY OF  
TECHNOLOGY


# **COS10004 Computer Systems**

## **Lecture 2.1 – More Adders and Programmable Gates**

CRICOS provider 00111D


*Chris McCarthy*

# Half-adder

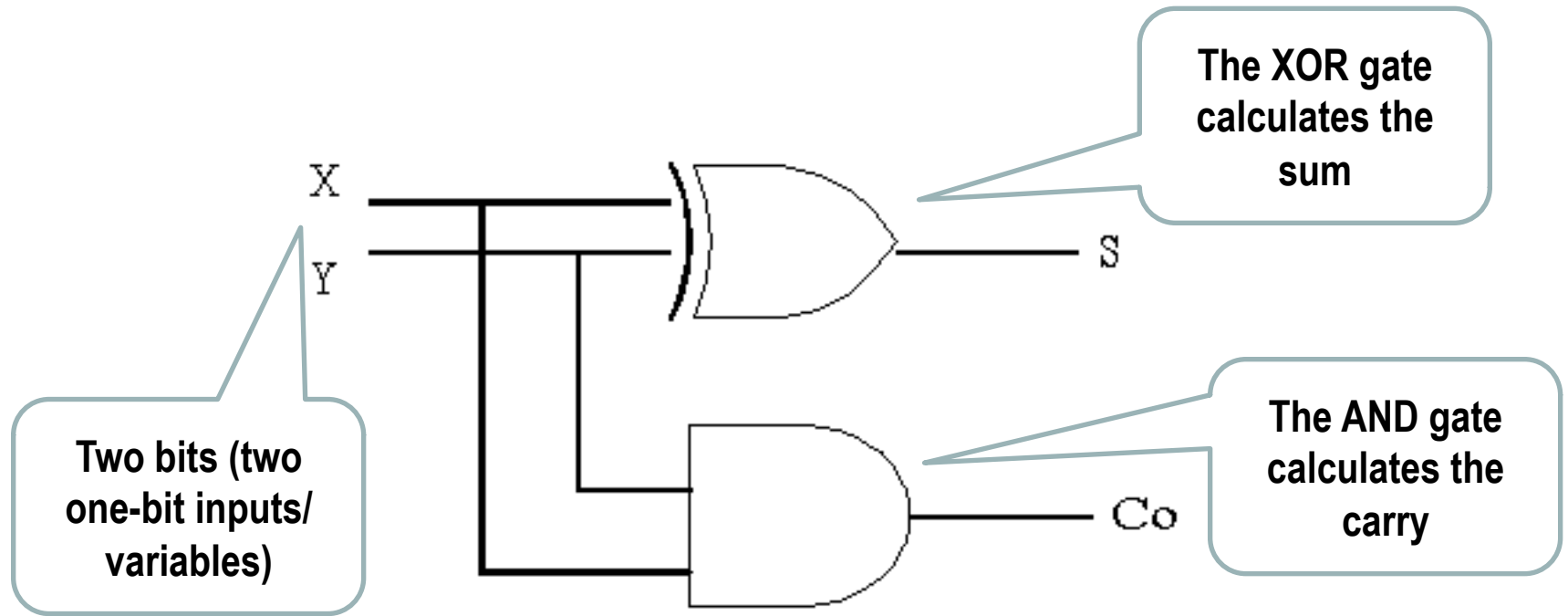


# A full adder


> Made from two half-adders:

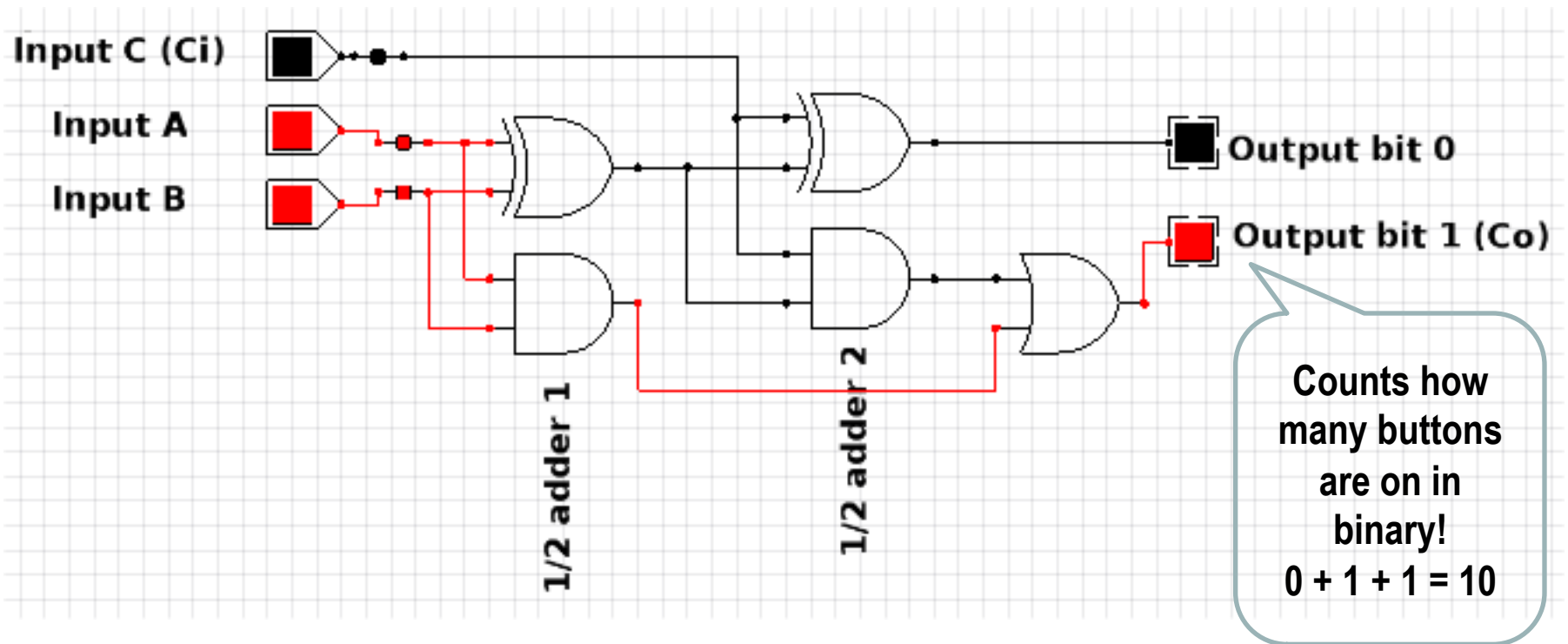

## Full adder sum only

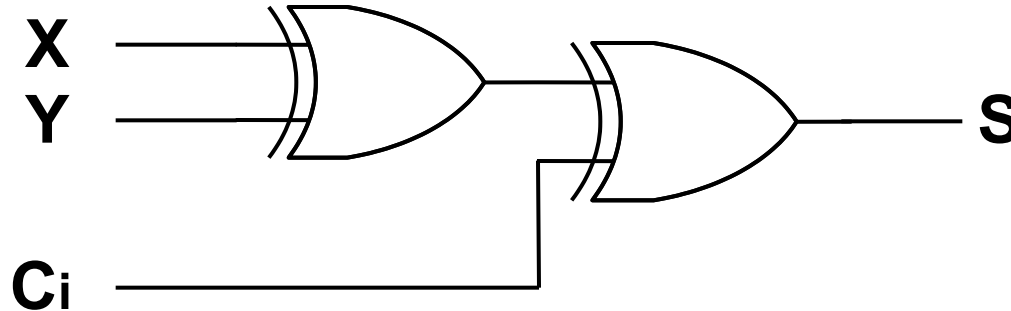

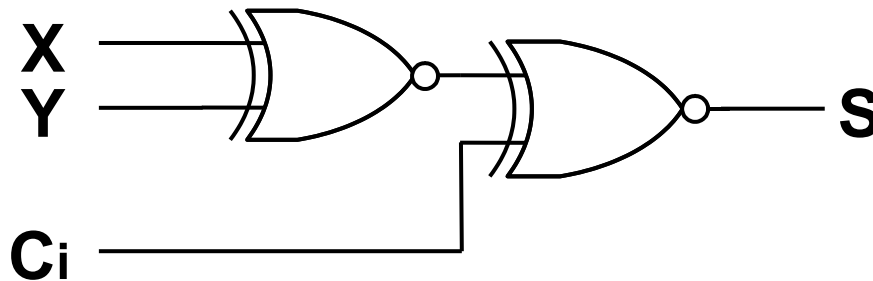The following with two XNOR gates also works – check both using the simulator.




# 1-BIT FULL ADDER? BUT THAT'S JUST ADDING TWO BITS


To add real numbers together (8 bits, 16, 32...) we need to cascade full adders together.

Use a half adder for the first bits, full adders for the other 7 (15, 31...)



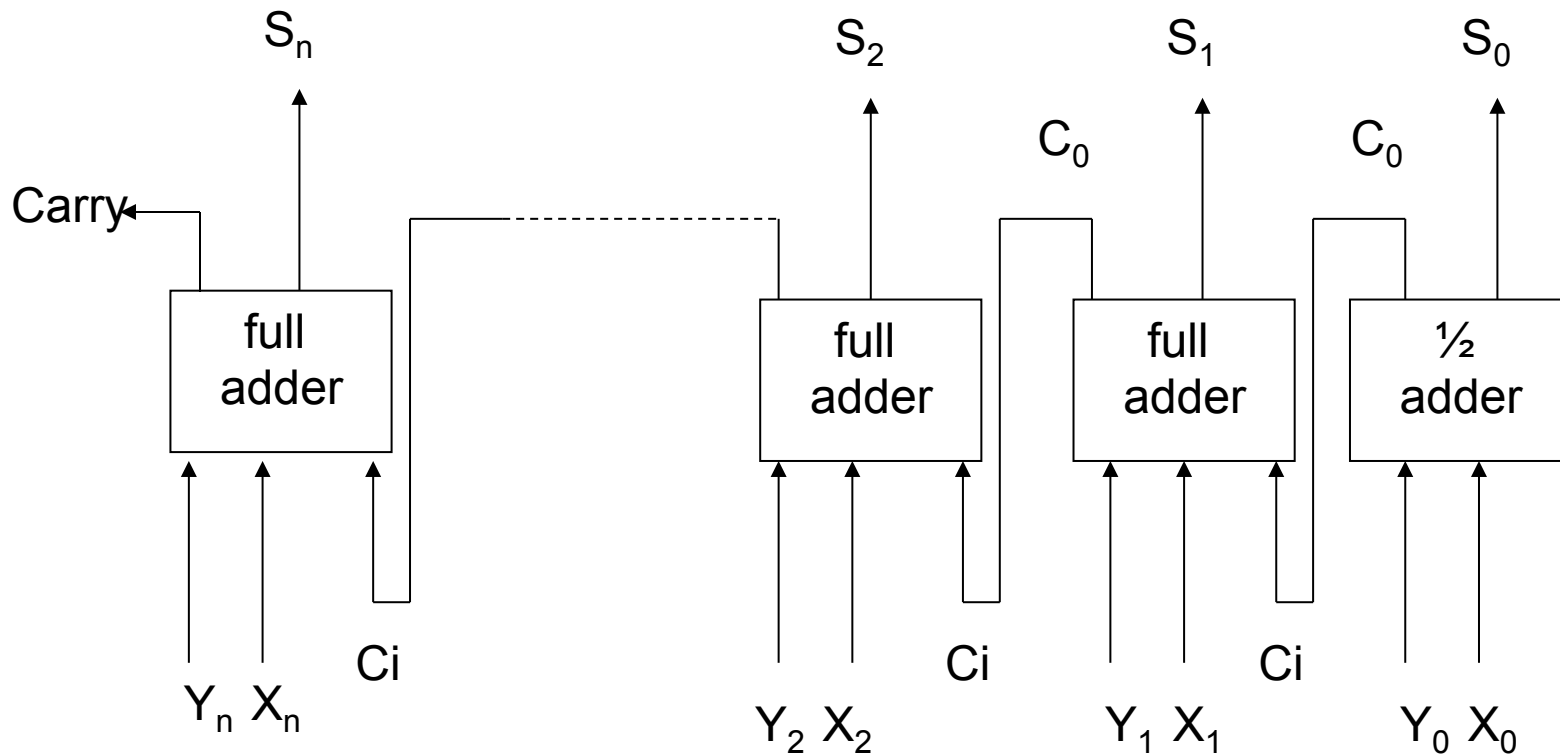Multi bit addition - combine 8 adders with carry to get 8-bit addition (of two 8-bit numbers).



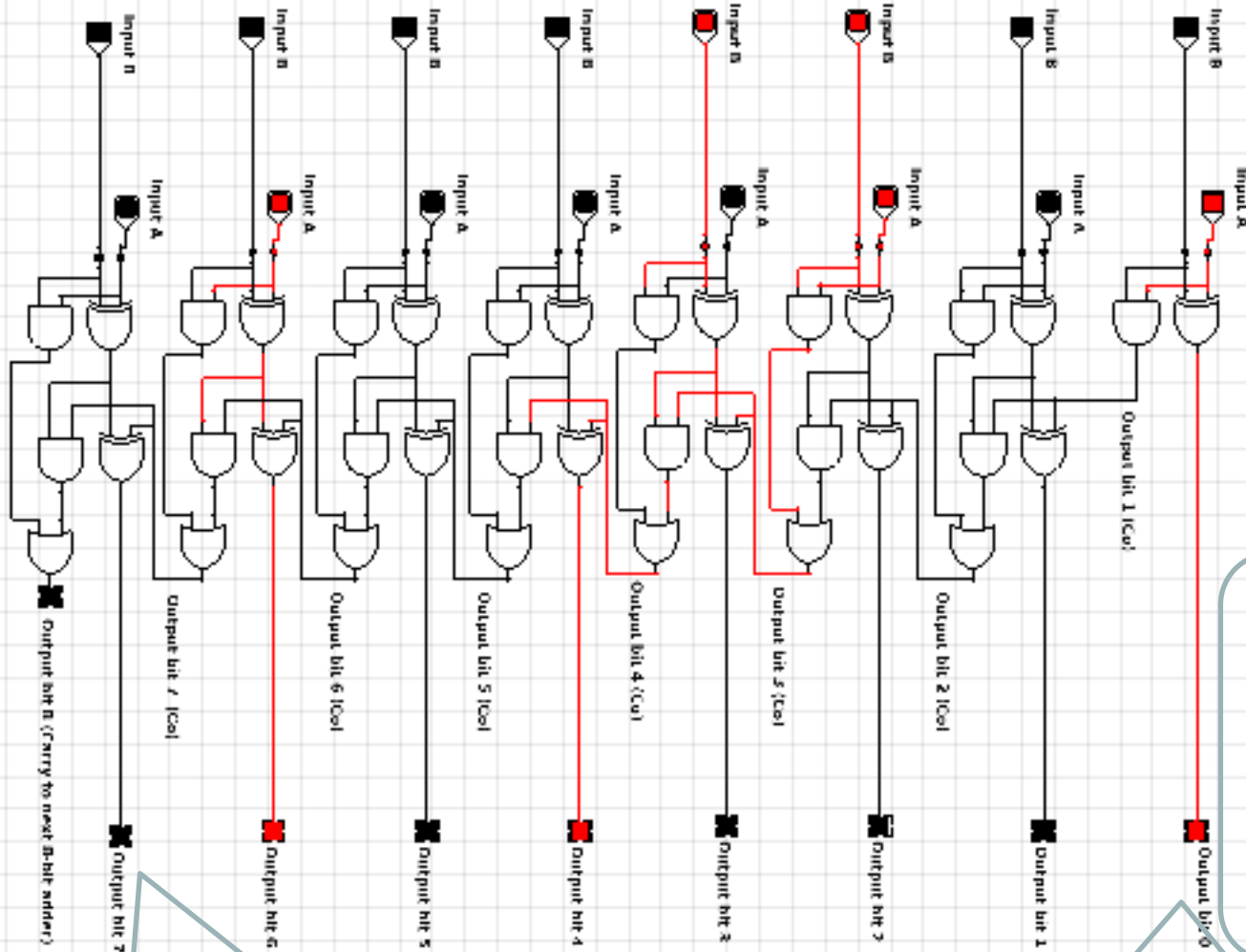

**A = 69**  
**B = 12**  
**Output =**  
**69 + 12 =**  
**81**

**A = 0x45**  
**B = 0x0C**  
**Output =**  
**0x51 = 81**

**Most-significant bit ( $2^7$ )**

**Least-significant bit ( $2^0$ )**

# A BIT MORE ABOUT GATES

---


Some gates offer useful functionality that is not immediately obvious

Lets look at a couple of examples ...


---




# USING XOR AS A CONTROLLED INVERTER

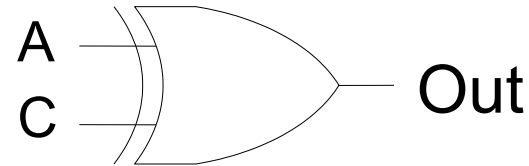

C	A	Out
0	0	0
0	1	1
1	0	1
1	1	0

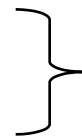

If C=0, output = A

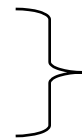


If C= 1, output =  $\overline{A}$

"to invert or not invert..."


It's like  
turning **on** C  
enables the  
inverter  
(Out=  $\overline{A}$ )

# AND AS A LOGIC-CONTROLLED SWITCH

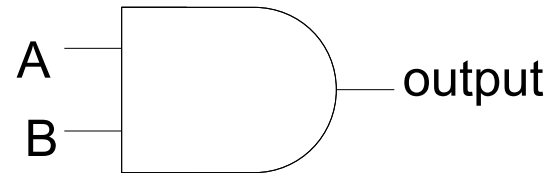

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

# AND AS A LOGIC-CONTROLLED SWITCH

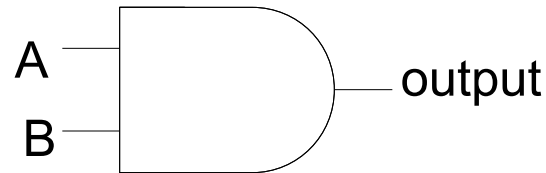

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

AND gate as a switch


If A=0, output always 0

If A=1, output = B

To pass through B, or not to pass through B ?  
.... A is the question.

It's like turning on A  
enables the output being B  
(0 = B)

# Choose which circuit forms the output

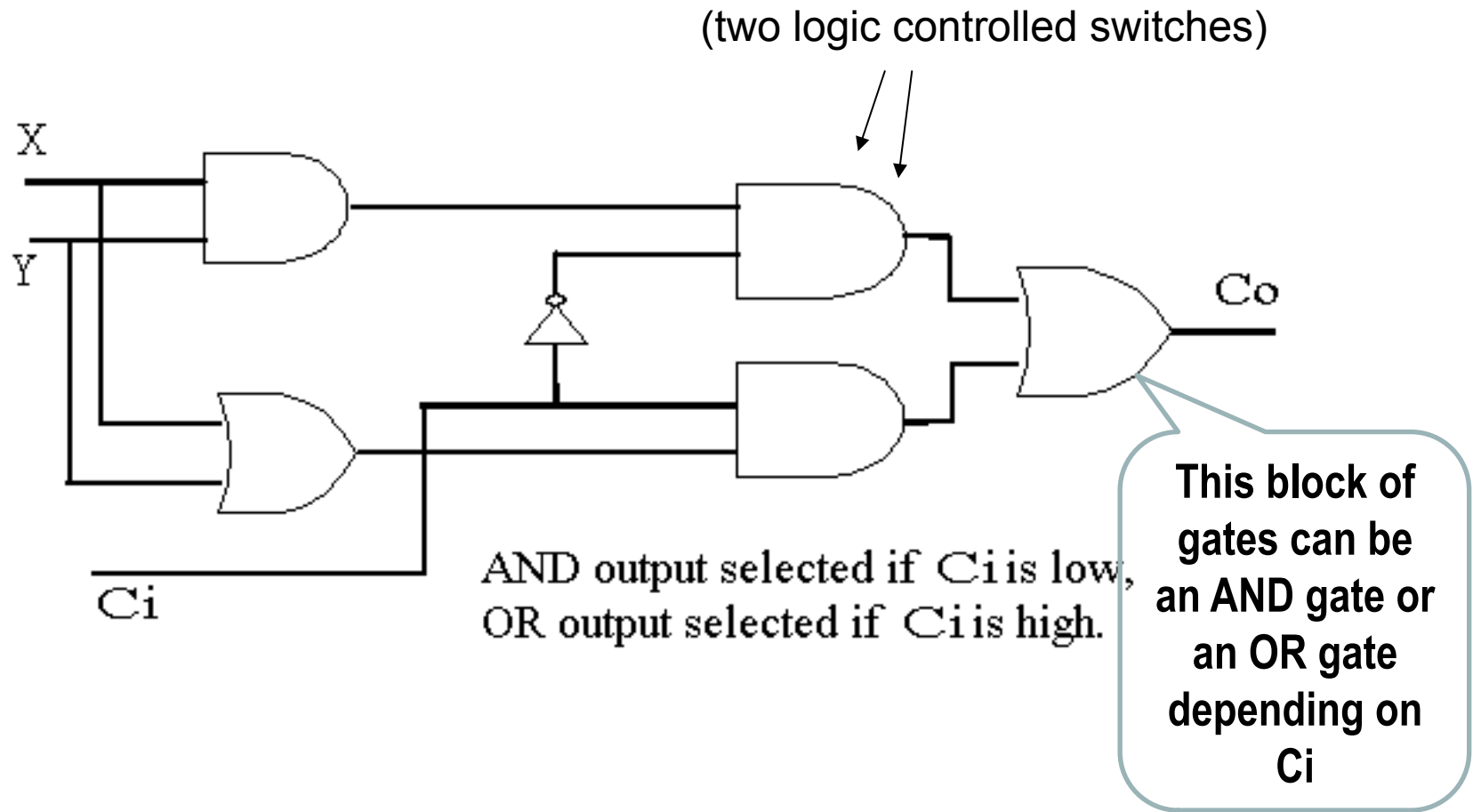


# WAIT A MINUTE !

... you're saying we have the capability to Program the behaviour of a block of gates ?



# Yep

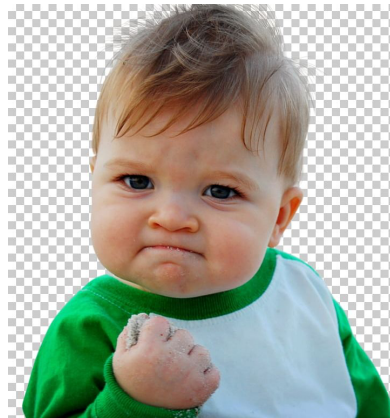

# YES - Programmable Gates!

We can program a gate to be an inverter or a buffer.

We can program a gate to do AND or OR.



# SUMMARY

---

Full Adders can combine to create full scale addition machines

Gates offer programmability using control bits

- this can be very useful for controlling data flow

Next Lecture: Clocks for synchronised.